

CSE251 - Section - 22

Assignment - 03

Name: Anupam Sen Sagon

ID : 22299049

Date : 15<sup>th</sup> December, 2024

Answer to the Question No-01  
(Full-wave)

(a)

$$V_s(t) = 7 \sin(400\pi t)$$


$$\omega = 400\pi$$

$$2\pi f_i = 400\pi$$

$$f_i = 200 \text{ Hz, } f_r = 2 \times 200$$

(Input) = 400 Hz  
(output)

(b)

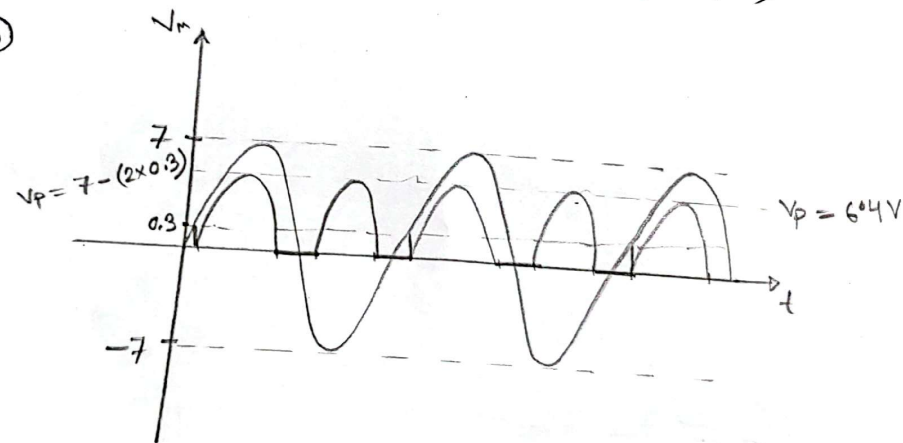

(c)

$$V_{DC1} = V_{avg} = \frac{2V_m}{\pi} - 2V_{D0}$$
$$= \frac{2 \times 7}{\pi} - (2 \times 0.3)$$
$$= 3.856 \text{ V.}$$

After connecting a capacitor,  $C = 100 \mu F$

(d) Ripple voltage,  $V_r (P-P) = \frac{V_p}{f_r R C} = \frac{V_m - (V_{D_o} \times 2)}{f_r R C}$

$$= \frac{7 - (2 \times 0.3)}{400 \times 5 \times 10^3 \times 100 \times 10^{-6}}$$
$$= 0.032$$

(e)  $V_{DC_2} = V_p - \frac{V_r}{2}$

$$= \{7 - (2 \times 0.3)\} - \frac{0.032}{2}$$
$$= 6.384 V$$

$$\Delta V_{DC} = V_{DC_2} - V_{DC_1} = (6.384 - 3.856)$$
$$= 2.528 V$$


(f) To make the rectifier output smoother, add a bigger capacitor to reduce ripples, or use a combination of an inductor and capacitor for better results. In terms of getting more time constant ( $\tau$ ), the more get smoother dc signals.

(g) The frequency of the Ripple voltage is 400 Hz.

Answer to the Question No-02  
(Full-wave)

(a)

$$V_i = 10 \sin(100\pi t)$$

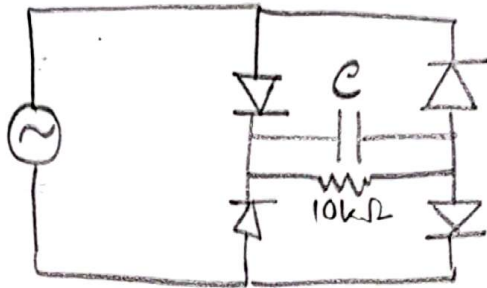

(b)

$$\text{peak output voltage, } V_p = \{10 - (2 \times 0.8)\}$$

$$= 8.4 \text{ V}$$

$$\text{peak to peak ripple voltage, } V_{r(p-p)} = \frac{3}{100} \times V_p$$

$$= \frac{3}{100} \times 8.4$$

$$= 0.252 \text{ V}$$

(c)

$$V_{DC} = V_{avg} = V_p - \frac{V_r}{2}$$

$$= 8.4 - \frac{0.252}{2} = 8.274 \text{ V}$$

(d)

$$V_r = \frac{V_p}{f_r RC}$$

$$\Rightarrow 0.252 = \frac{8.4}{100 \times 10 \times 10^3 \times C}$$

$$\Rightarrow C = 3.33 \times 10^{-5} \text{ F}$$

Capacitor

$$V_m = 10 \text{ V}$$

$$\omega = 100\pi$$

$$2\pi f_i = 50 \text{ Hz}$$


$$f_r = 100 \text{ Hz}$$

10. Answer to the Question No-03


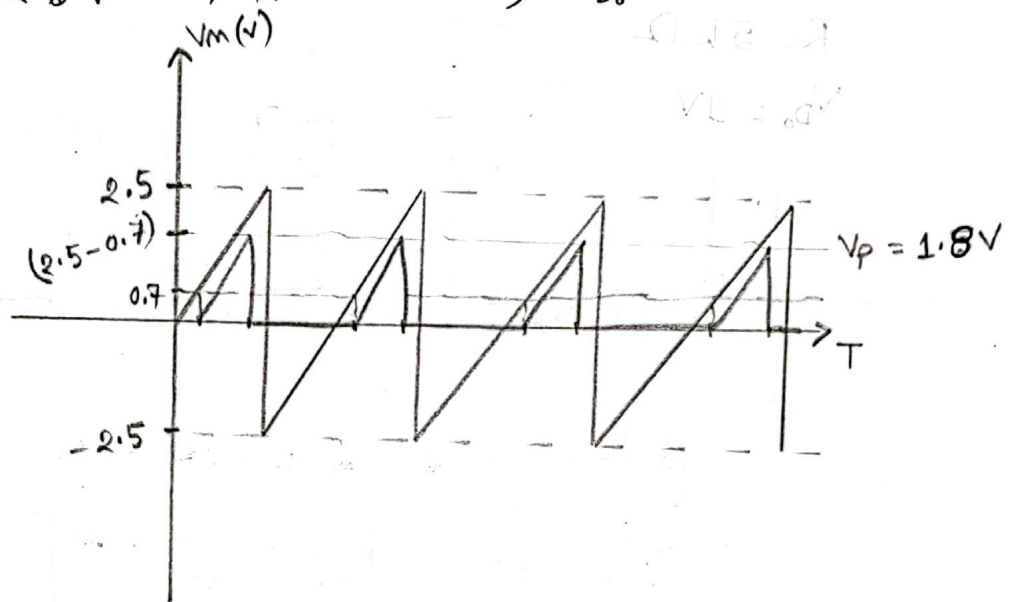
(a) (Half-wave)  $\rightarrow$  Triangular-wave

$$V_i(p-p) = 5$$

$$V_m = 2.5V, R = 1K\Omega, V_{D_0} = 0.7V$$



(b)

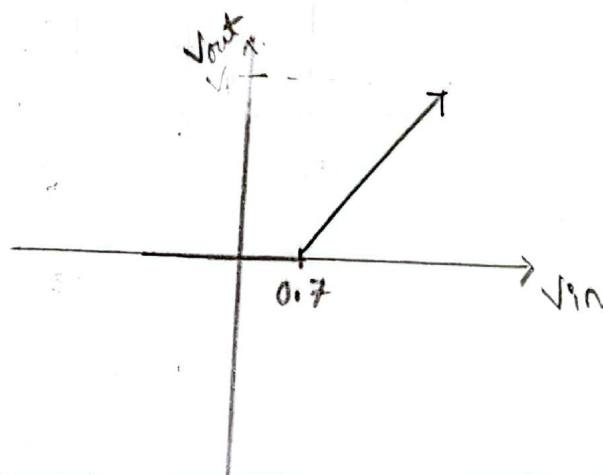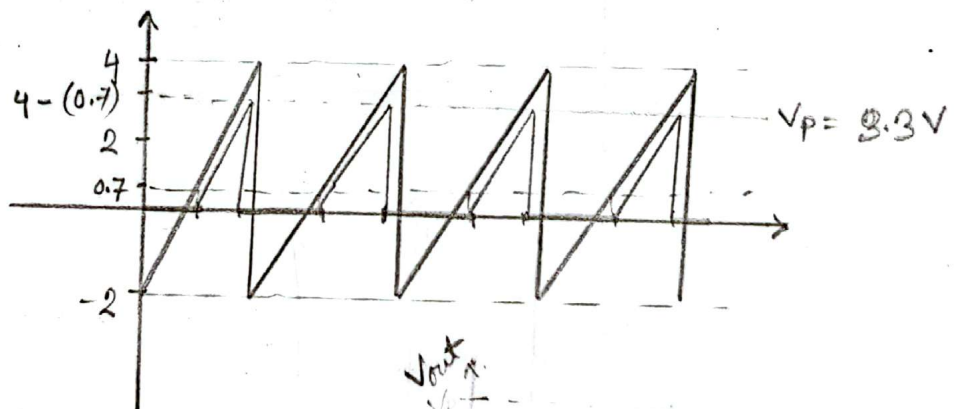



Answer to the Question No-04  
(Half-wave - Square)

(a)


$$V_m = 15$$

$$f_i = 0.5 \text{ Hz}$$


$$R = 5 \text{ k}\Omega$$

$$V_{D_0} = 1 \text{ V}$$


VTC: -

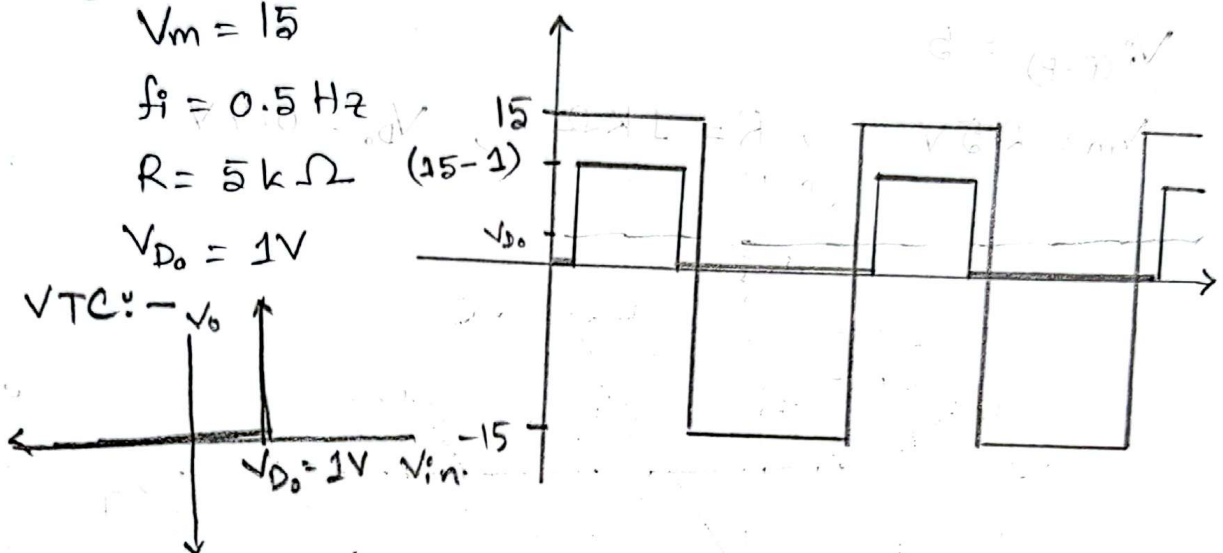

(b)

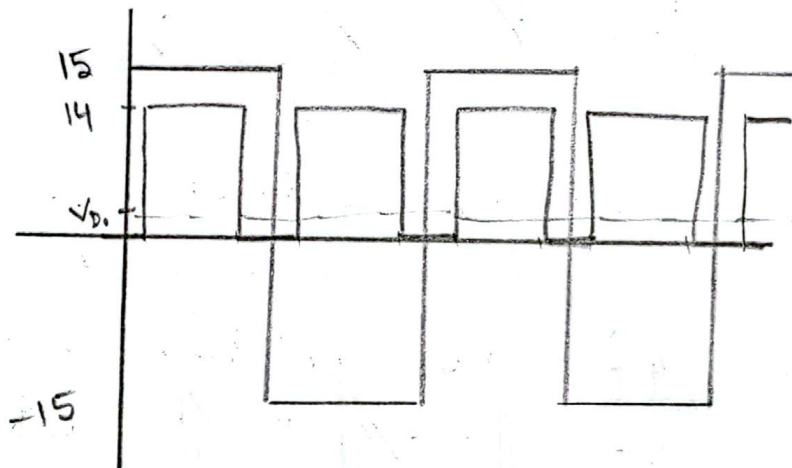


VTC

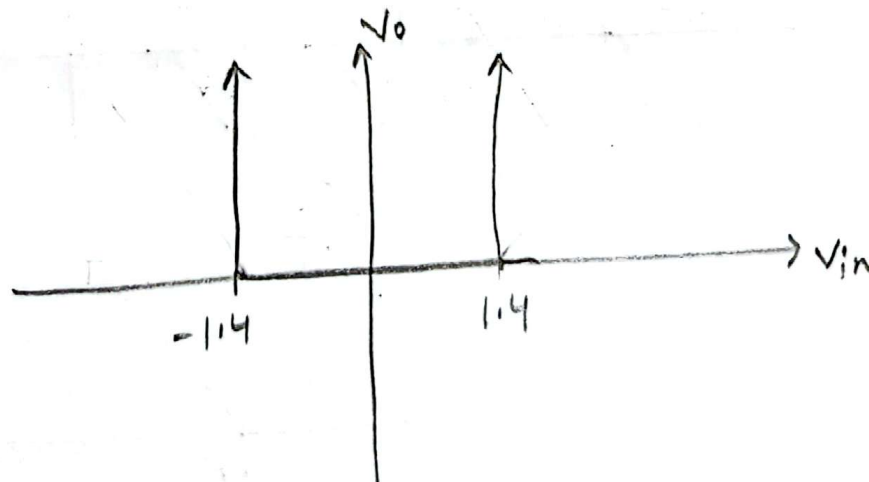

Answer to the Question No-05  
(Full-wave with Capacitor)

(a)

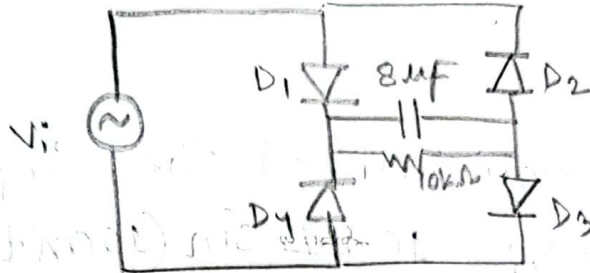

(b)

$$R = 10 \times 10^3 \Omega, \quad C = 8 \times 10^{-6} F$$

$$I_{avg} = 0.75 \text{ mA} \quad f_r = 100 \text{ Hz} \quad f_i = 50 \text{ Hz}$$

$$V_{D_0} = 1 \text{ V}$$

$$V_{avg} = I_{avg} \times R = 0.75 \times 10^{-3} \times 10 \times 10^3 = 7.5 \text{ V}$$

We know,

$$V_{avg} = V_p - \frac{V_r}{2}$$

$$\Rightarrow 7.5 = (V_m - 2V_{D_0}) \left(1 - \frac{1}{2 \times 100 \times 10 \times 8 \times 10^{-3}}\right)$$

$$\Rightarrow V_m - 2V_{D_0} = 8.5 = V_p$$

$$\Rightarrow V_m = 8.5 + 2V_{D_0}$$

$$V_m = 10.5 \text{ V}$$


$$\omega = 2\pi f_i$$

$$= 2\pi \times 50$$

$$\omega = 100\pi$$

So, the equation of the input waveform  $\Rightarrow V_i = 10 \sin(100\pi t)$

©

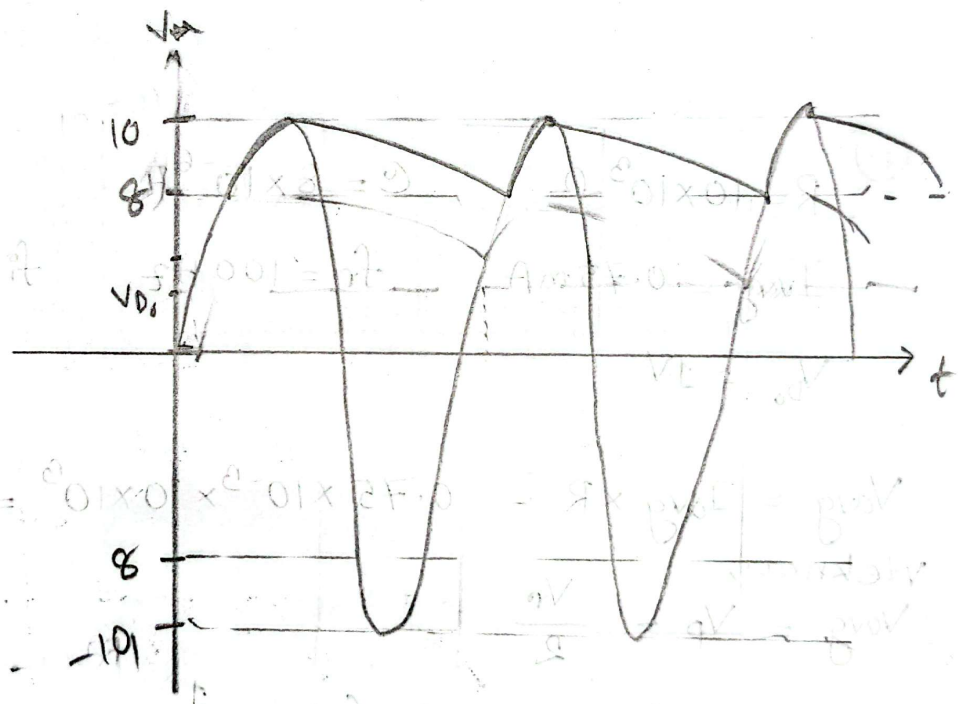

$$\left( \frac{0.01 \times 8 \times 0.1 \times 100 \times 10^3}{1} \right) (1 - 1) = 0 \text{ V} \Rightarrow$$

$$V = 10 \text{ V} = 10 \text{ V} \Rightarrow$$

$$V = 10 \text{ V} + 10 \text{ V} = 20 \text{ V} \Rightarrow$$

$$V = 10 \text{ V} = 10 \text{ V}$$