

Set 01

1.(a) Assumptions for the parameters of an ideal op-amp -

i) Infinite open loop gain. 0.5

ii) Infinite input resistance. 0.5

no partial marks here

iii) Zero output resistance. 0.5

(b) $V_o = -\frac{1}{RC} \int V_i dt$ 1 no partial marks here

(c) Because of non-linear I-V characteristic.

no partial marks here

(d) F.B:-
1 $i_D > 0$

R.B:-
1 $V_D \leq V_{DO}$

no partial marks here

Set 02

1. (a) Same as 1(a) [Set 01]

(b) $V_o = -RC \frac{d}{dt} V_i$

(c) Same as 1(c) [Set 01]

Same as Set-01

(d) F.B:-
 $i_D > 0$


R.B:-
 $V_D \leq 0$

Set-01


Calculation of V_x - 1
Waveform drawing - 3
Graph Label - 1

Q2

(a)

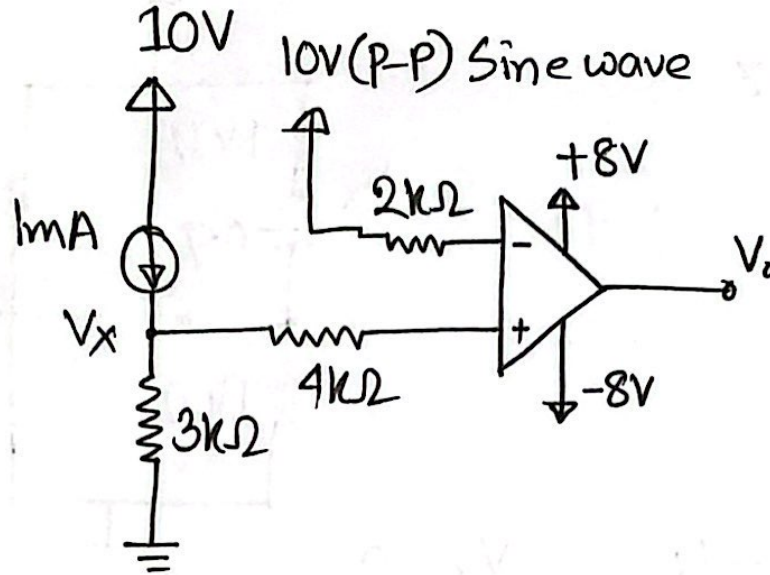

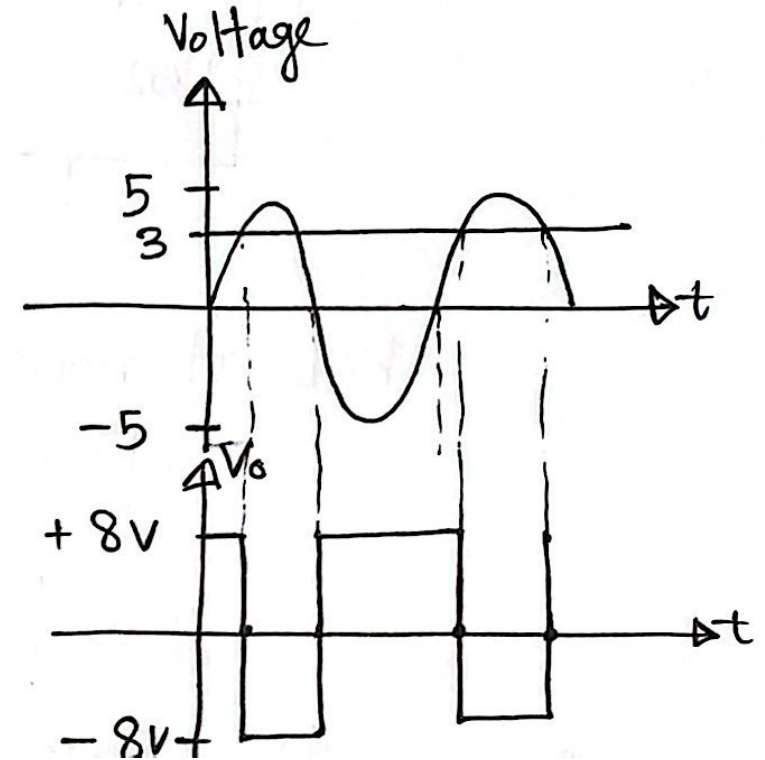
$$V_x = (1 \times 3) \text{ V} = 3 \text{ V}$$




(b)

$V_x - 1$
 $V_y - 1$
 $I_{D1} - 1$
 $I_{D2} - 1$

Validating
Assumption - 1

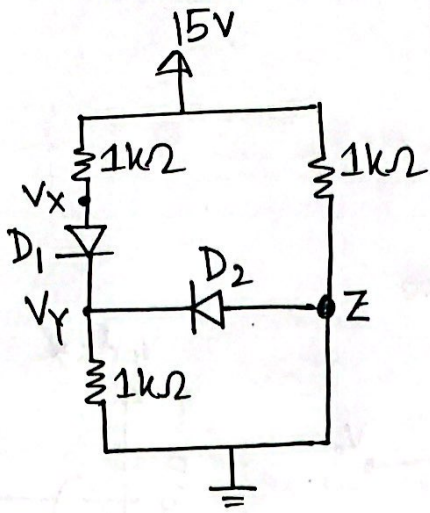

Assuming D_1 on and D_2 off

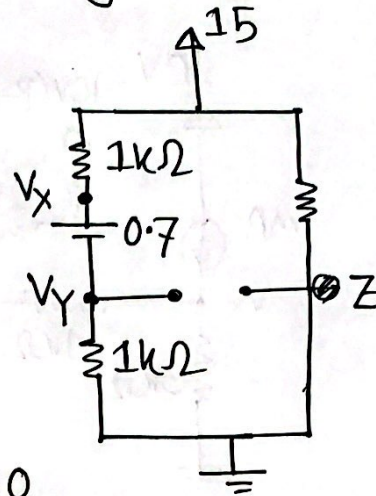

If the whole math is wrong due to a single variable, just penalize for that quantity & give the rest of the mark.

if the assumption is wrong but the process is ok, give 3 out of 5.

KCL at node Y-

$$\frac{15 - 0.7 - V_Y}{1} = \frac{V_Y - 0}{1}$$

$$\Rightarrow \boxed{V_Y = 7.15 \text{ V}} \quad \boxed{\therefore V_X = 7.85 \text{ V}}$$


Assumption validation:-

$$\boxed{I_{D1} = 7.15 \text{ mA}} \\ \boxed{I_{D2} = 0 \text{ mA}}$$

$$I_{D1} = \frac{15 - 7.15 - 0.7}{1} > 0$$

$$V_{D2} = V_Z - V_Y = 0 - 7.15 < V_{D02}$$

(c)

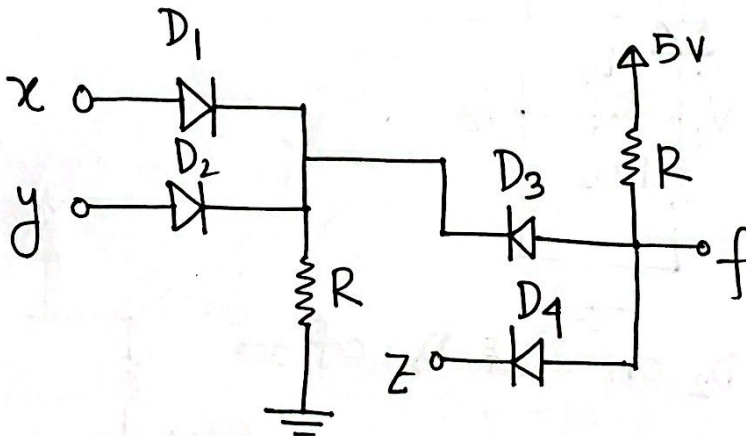

$$\boxed{f = (x \vee y) \cdot z} \quad \text{or} \quad \boxed{f = (x + y) \cdot z}$$

1






you can give 0.5 out of 1 if they can identify the OR gate / the AND gate but the function is not fully correct.

Q3

(a)


$$f = \frac{d^2x}{dt^2} + 10y + \int (10z - 9) dt$$

$\rightarrow T_3'$

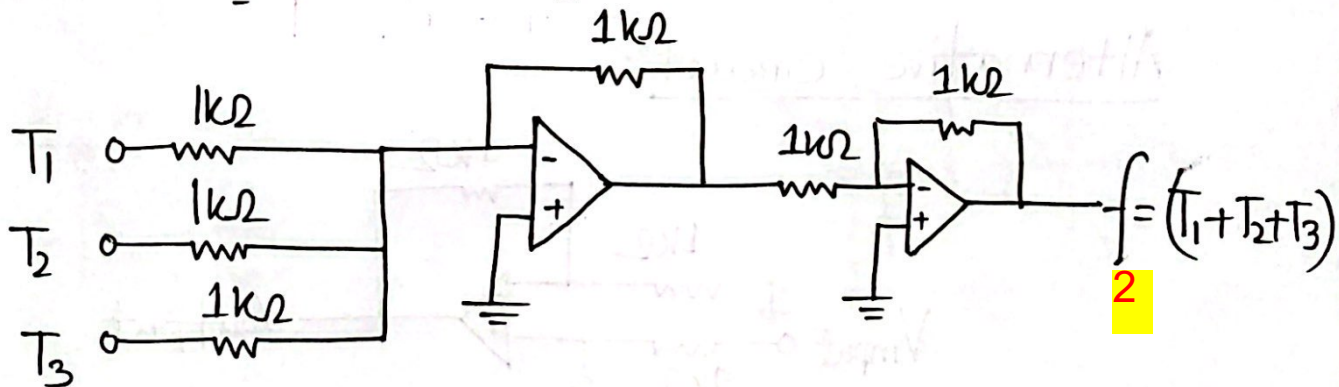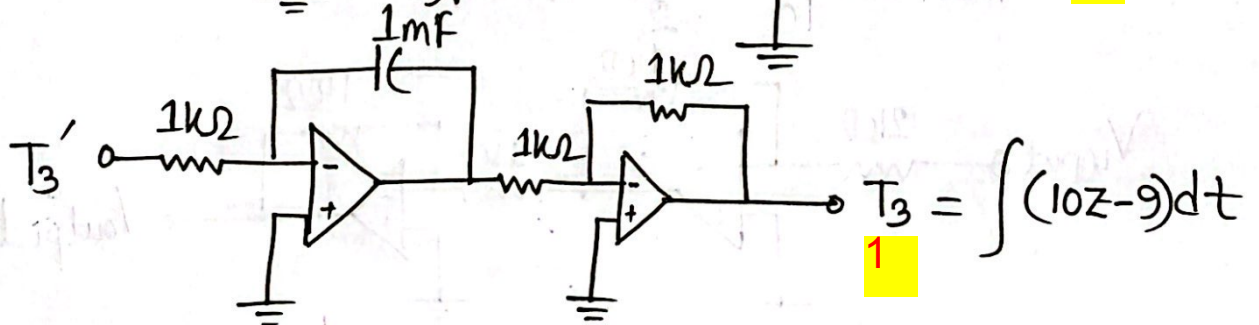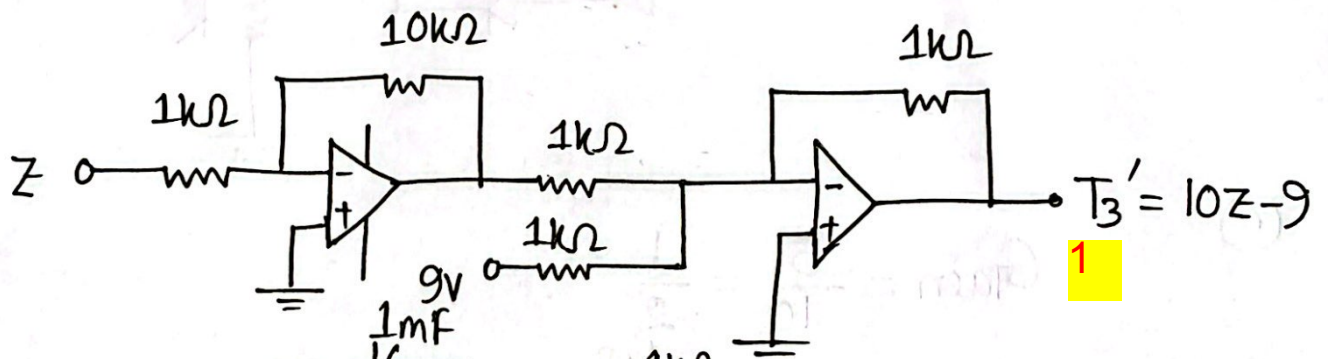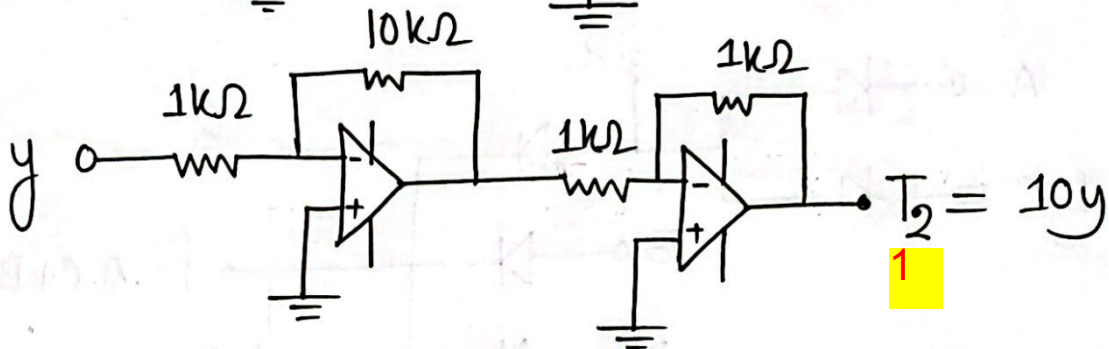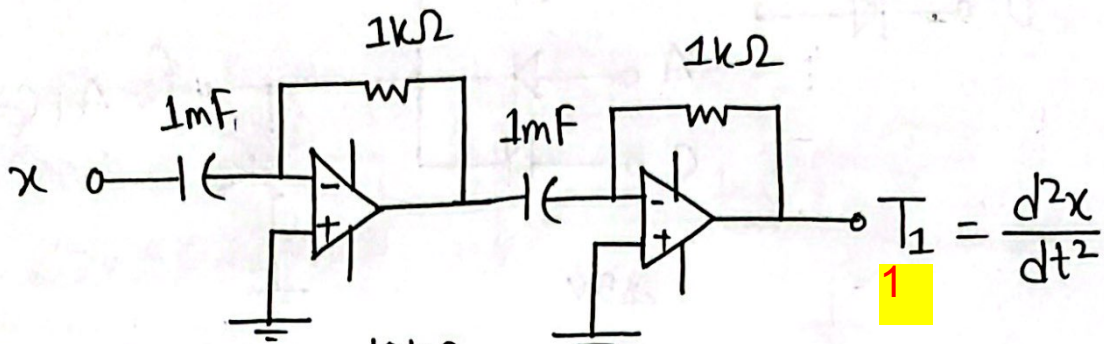


(b)

1.

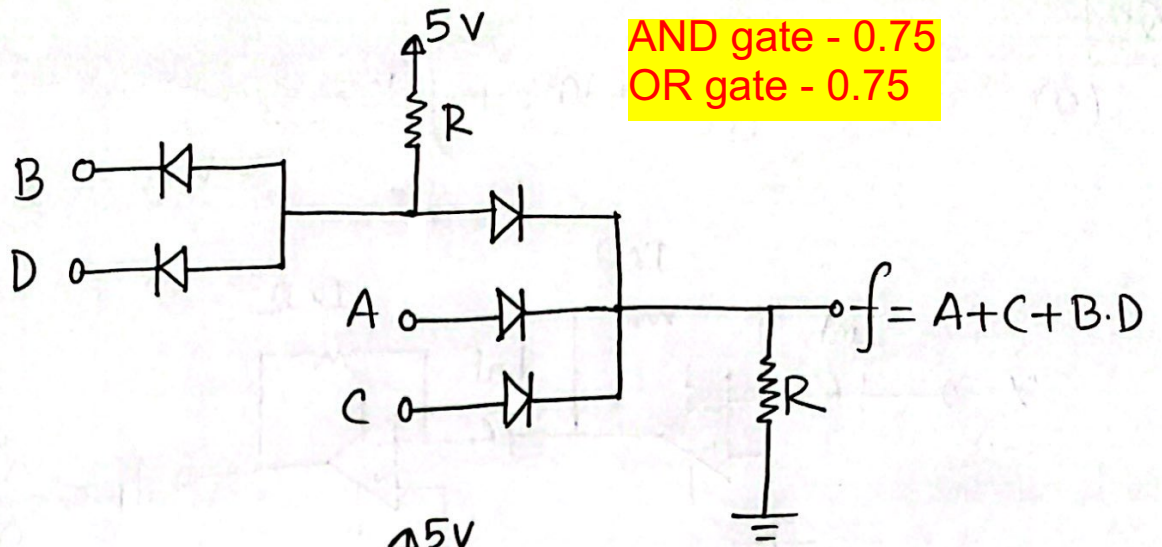

AND gate - 0.75
OR gate - 0.75

2.

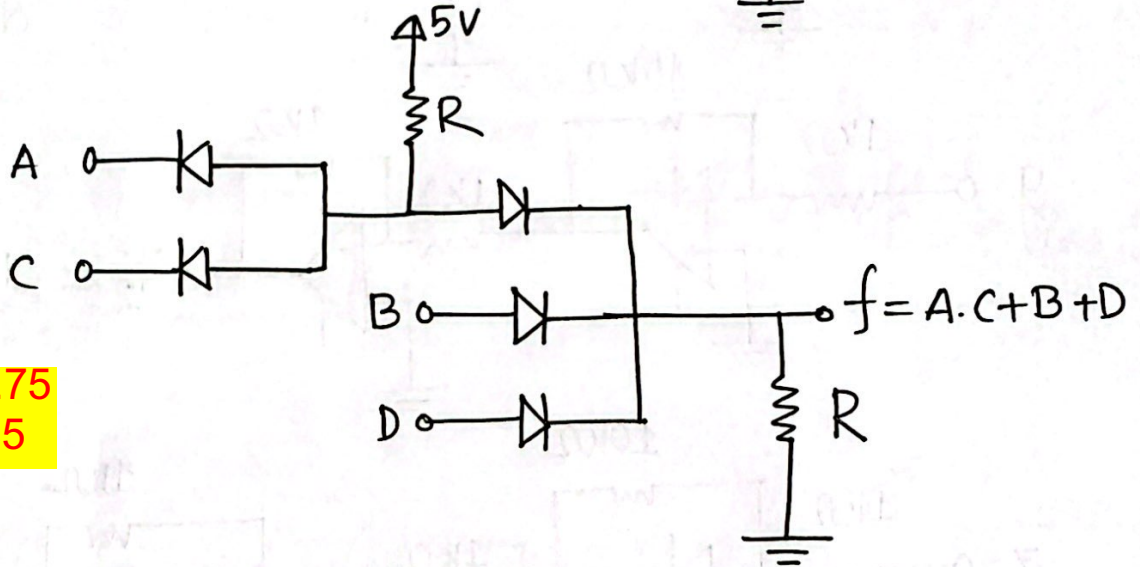


AND gate - 0.75
OR gate - 0.75


(c)

$$\text{Gain} = \frac{5}{10} = \frac{1}{2}$$

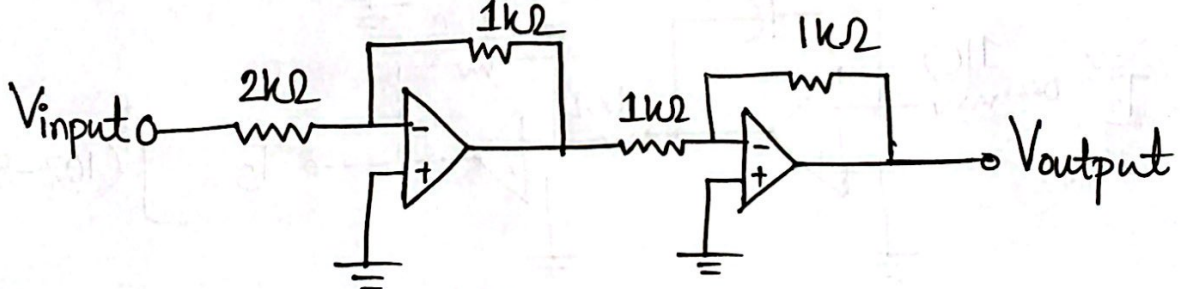Gain Calculation - 1
Ckt Implementation - 1



Alternative circuit:-

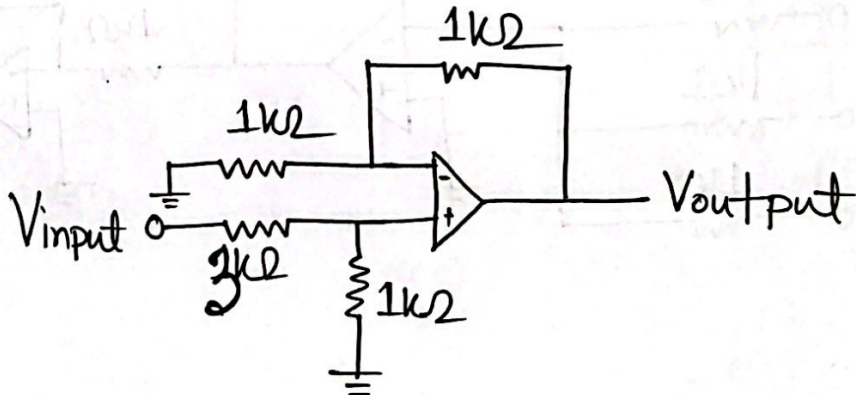


(d) $V_{\text{output(modified)}} = 2.5 + V_{\text{output}}$


A possible modification-

Equation Formulation - 1
Ckt Implementation - 1

Previous circuit:

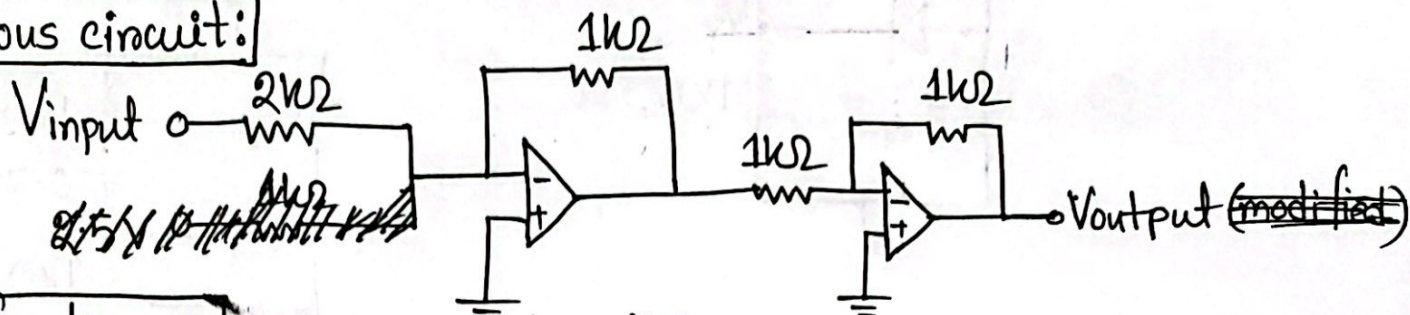


modifications:

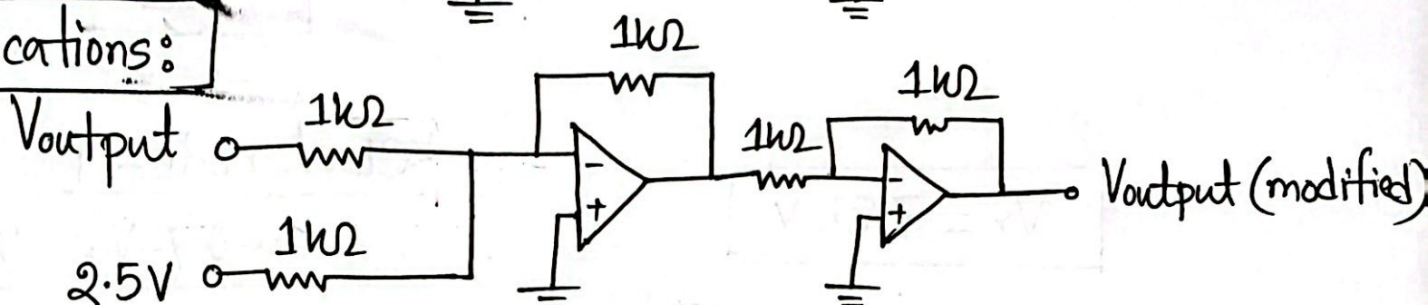

Set 02


SET-02 Evaluation Rubric will be similar to the one found in SET-01

2. (a)

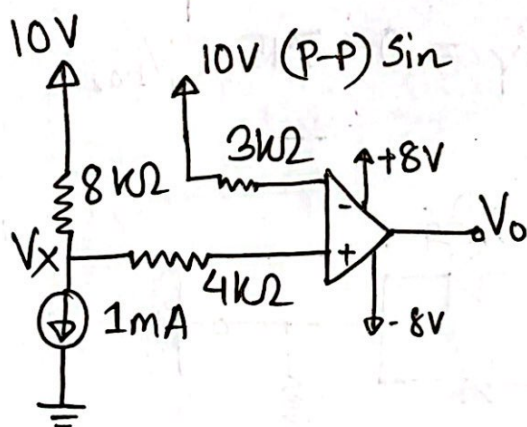


$$\frac{10 - V_x}{8} = 1$$

$$\Rightarrow V_x = 2V$$

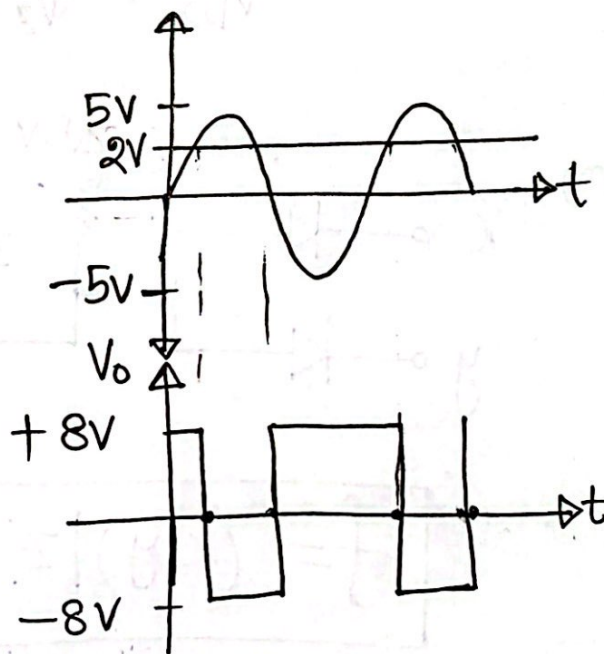

(b)

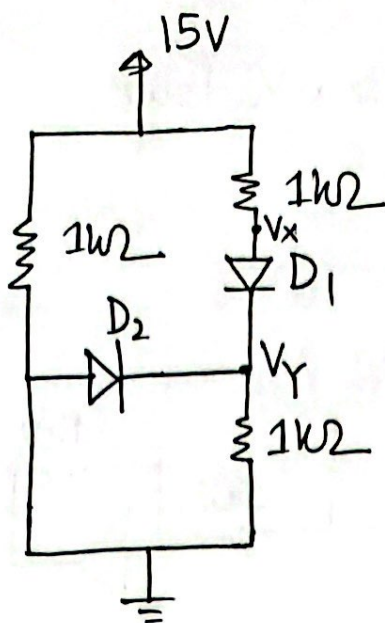

$$\therefore V_x = 7.85 \text{ V}$$

Assumption Validation:-


$$I_{D1} = \frac{15 - 7.15 - 0.7}{1} > 0$$

$$V_{D2} = V_z - V_y = 0 - 7.15 < V_{D02}$$

$$I_{D1} = 7.15 \text{ mA}$$

$$I_{D2} = 0 \text{ mA}$$

Assuming D_1 on and D_2 off

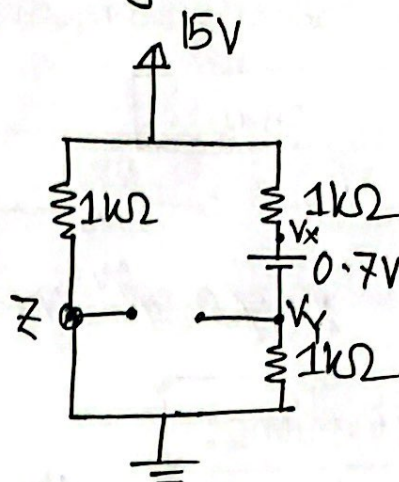


KCL at node - Y

$$\frac{15 - 0.7 - V_y}{1} = \frac{V_y - 0}{1}$$

$$\Rightarrow V_y = 7.15 \text{ V}$$






(c)

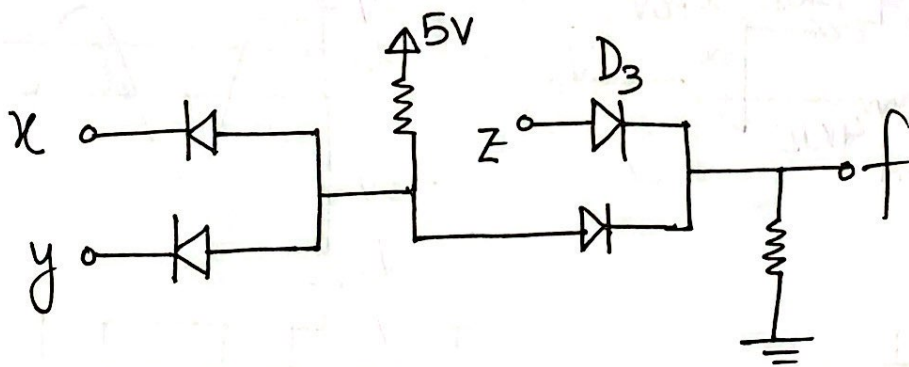



$$f = (x \cdot y) | z$$

$$\text{or } f = (x \cdot y) + z$$

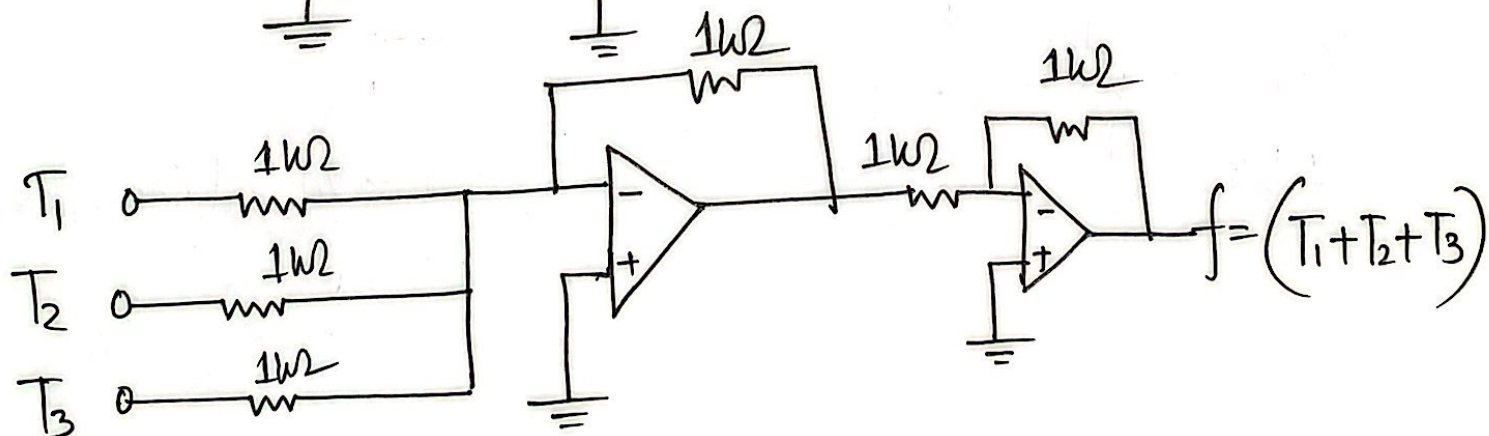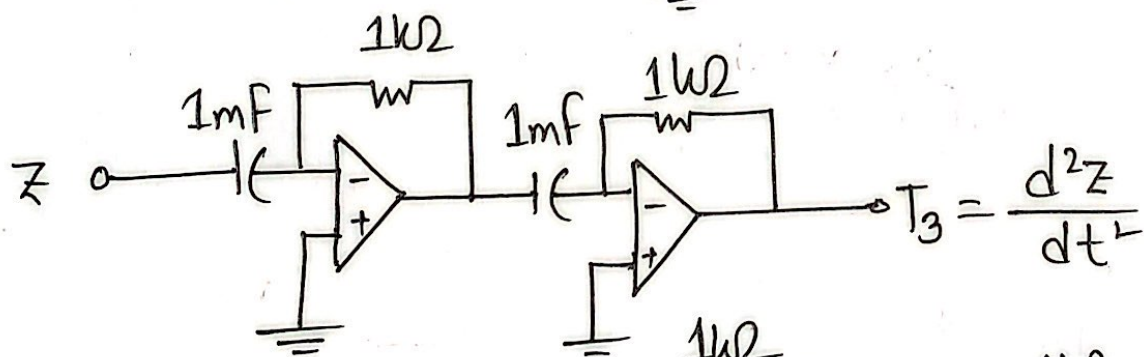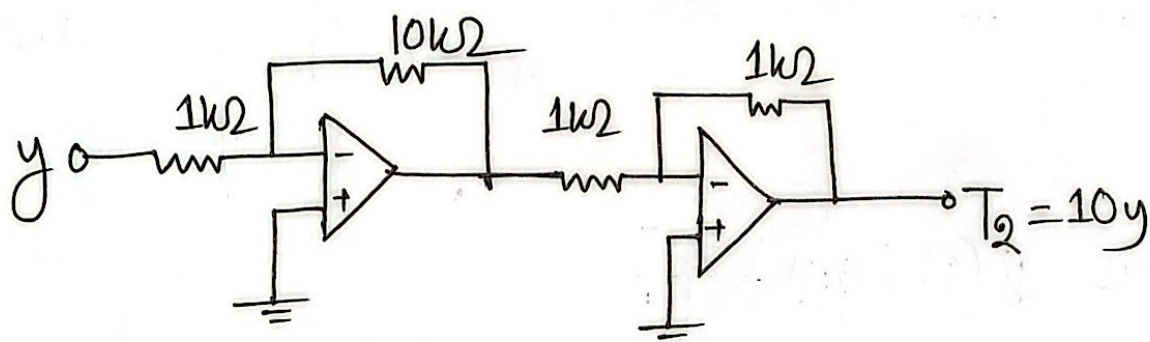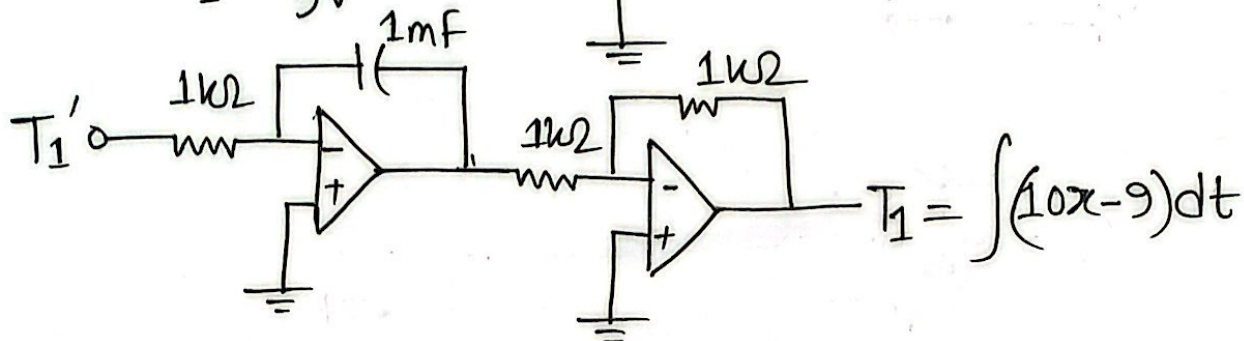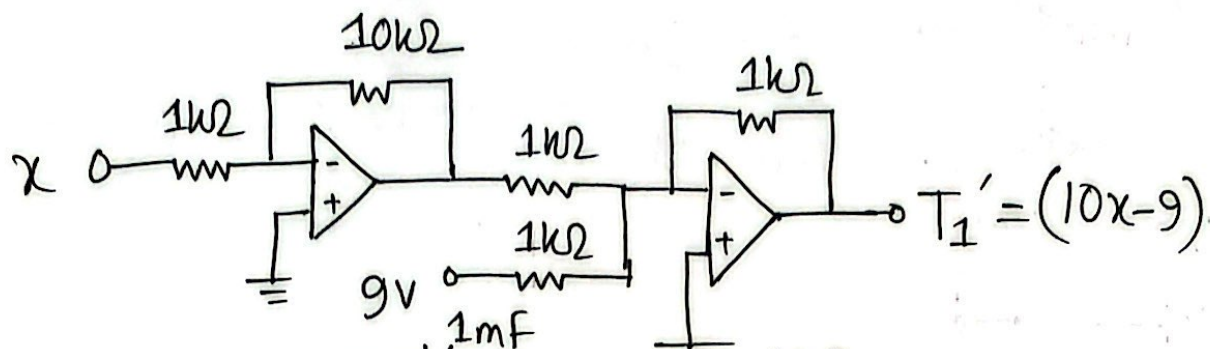Q3
(a) $f = \int \underbrace{(10x-9)}_{T_1'} dt + 10y + \frac{d^2z}{dt^2}$



b)

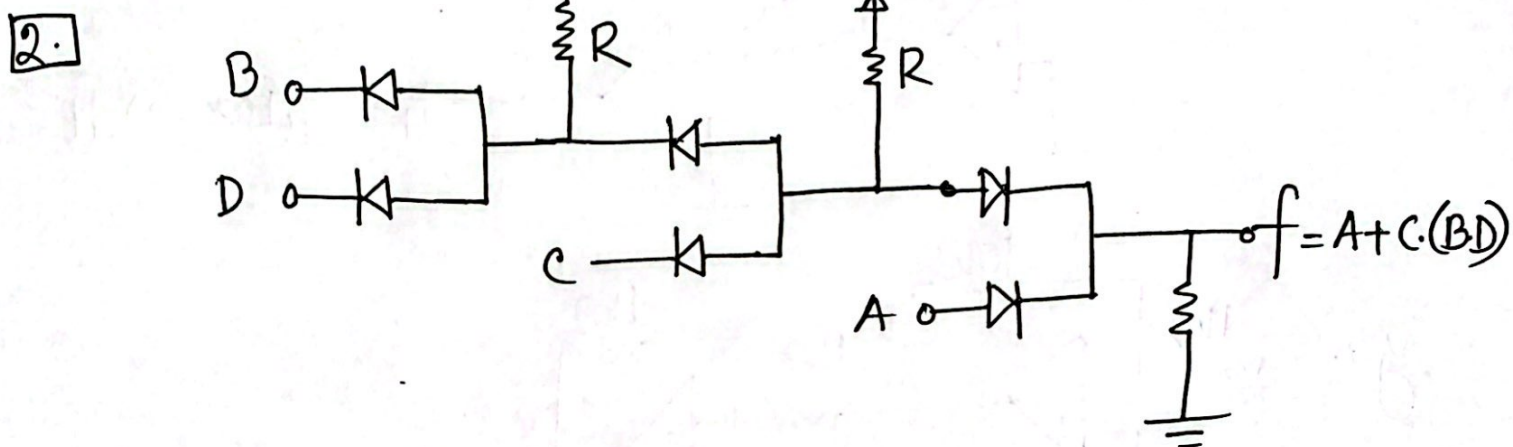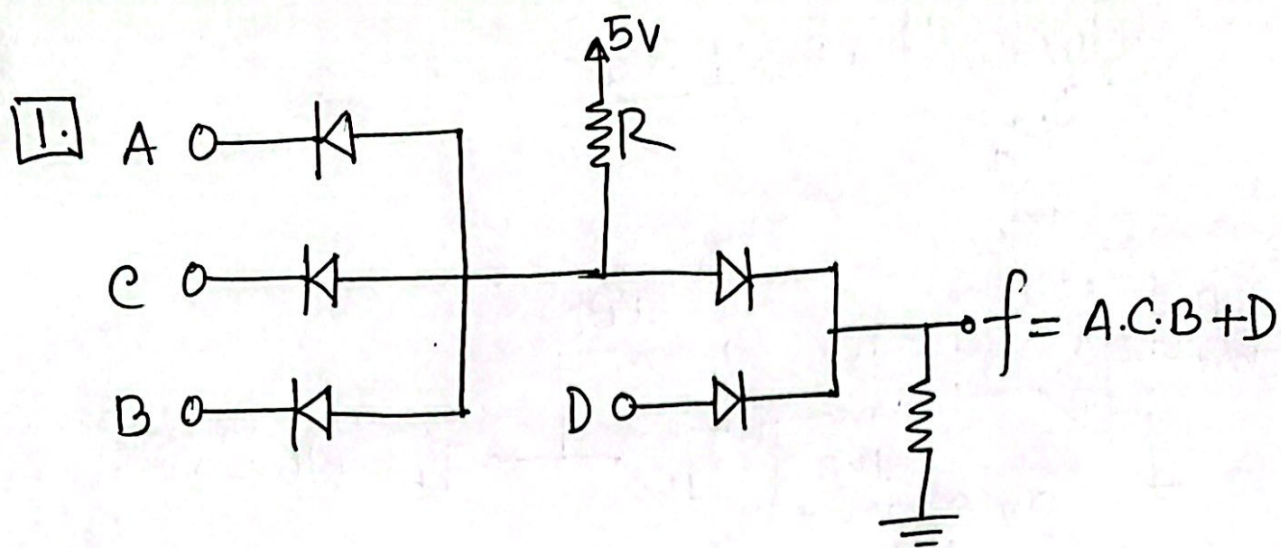

(c) same as 3(c) [set 01]

(d) $V_{output(mod)} = -2.5 + V_{output}$.

modifications:-

