

Lecture-1


KCL, KVL, Nodal Analysis & Line diagram


Alternative Circuit Representation: Line diagrams

Goal: representing circuits using Short hand notations


Steps

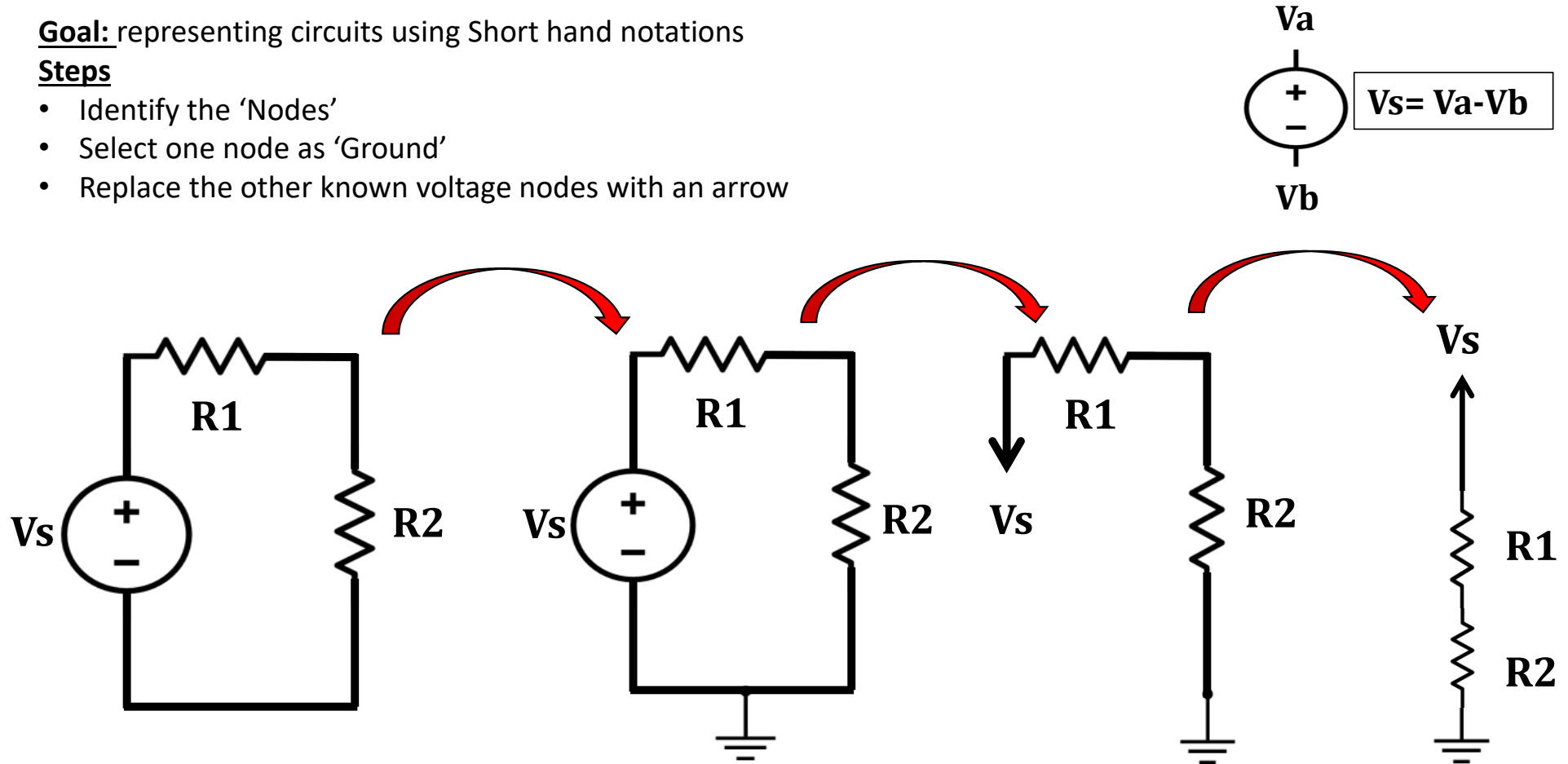- Identify the 'Nodes'
- Select one node as 'Ground'
- Replace the other known voltage nodes with an arrow



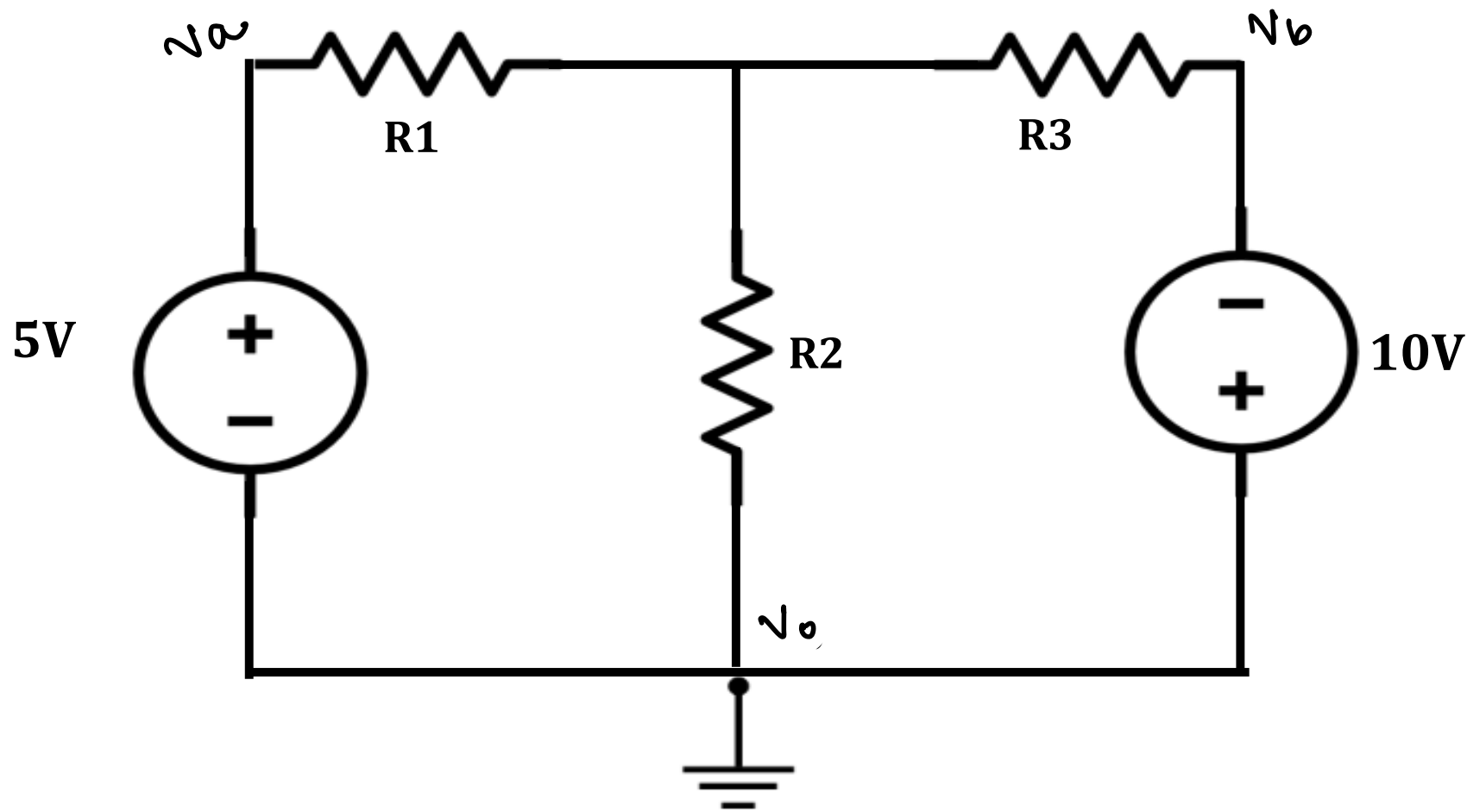

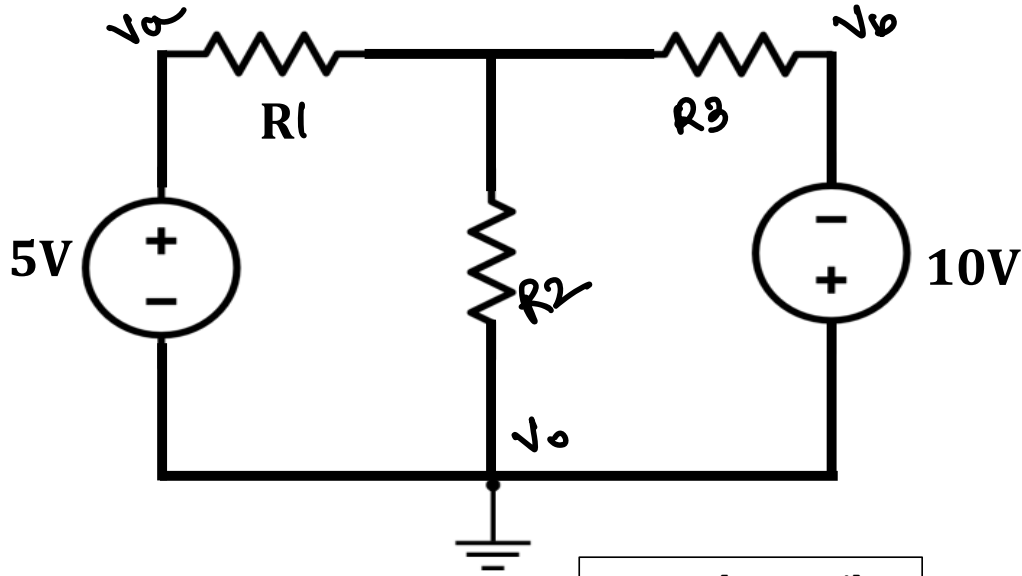- Circuits with voltage sources of opposite polarities



$V_o = 0V$ [Ground]

For 5V :



$$V_a - V_o = (5 - 0) V$$

$$\Rightarrow V_a = 5V$$



For 10V :

$$V_o - V_b = (0 - 10) V$$

$$\Rightarrow V_b = -10V$$

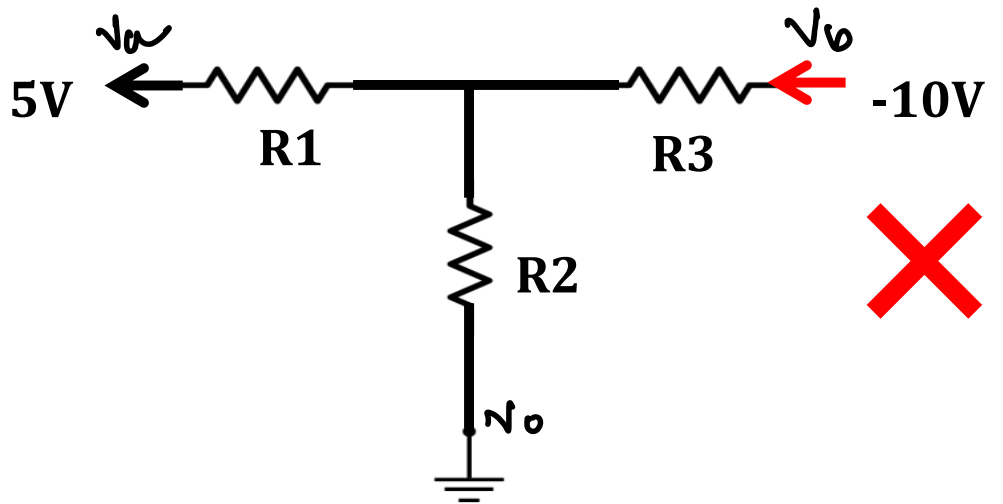
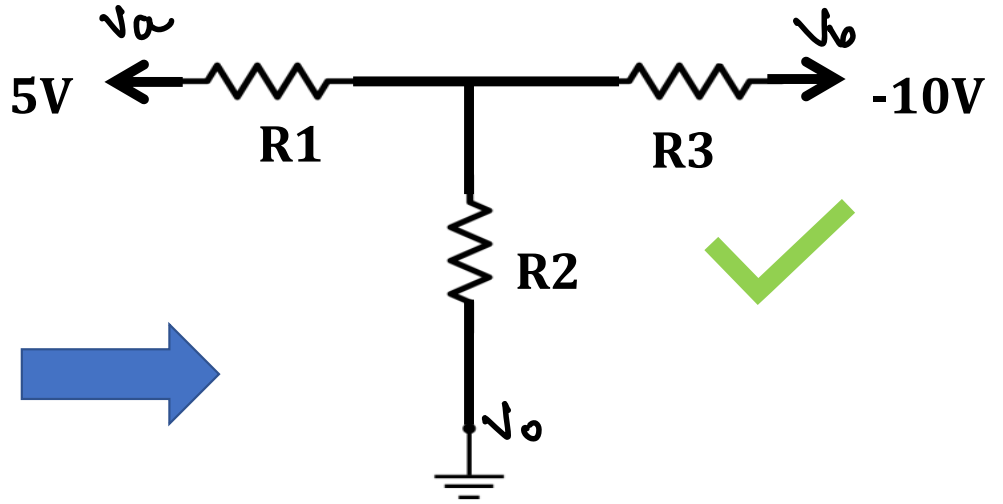


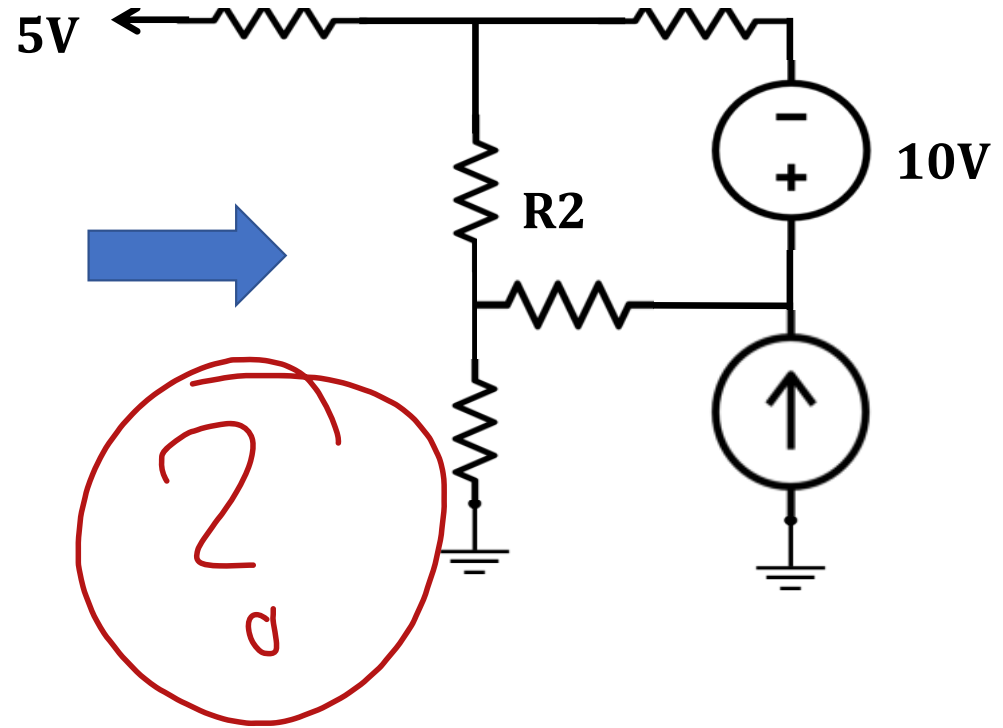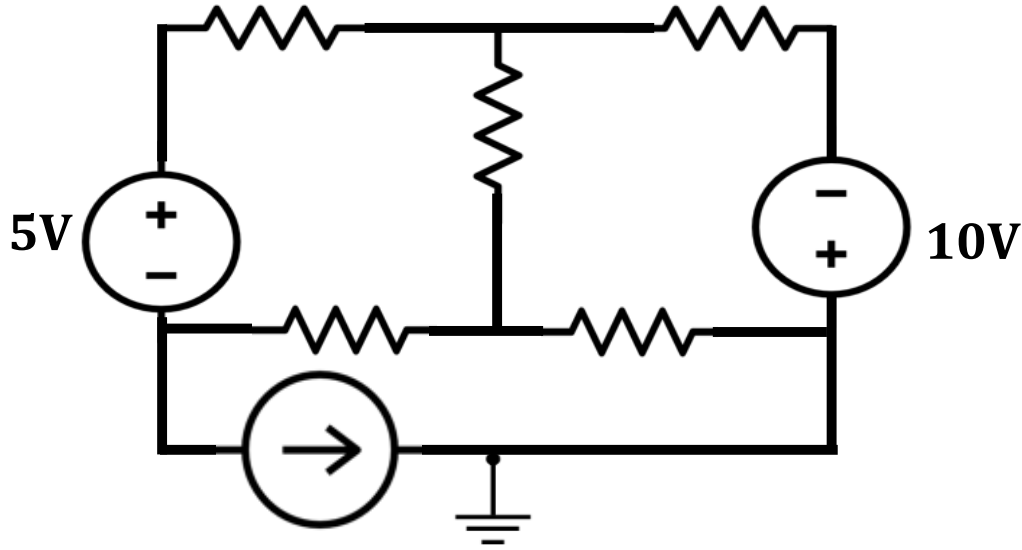- Circuit with a current source/ floating voltage source: Keep them as they are!
- **Floating voltage sources:** None of the terminals of the voltage source is connected to the reference i.e. ground node



Kirchhoff's Current Law (KCL):

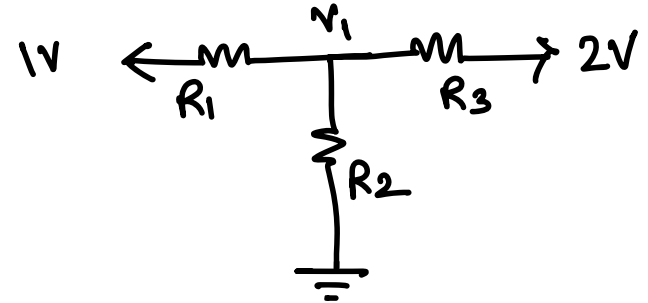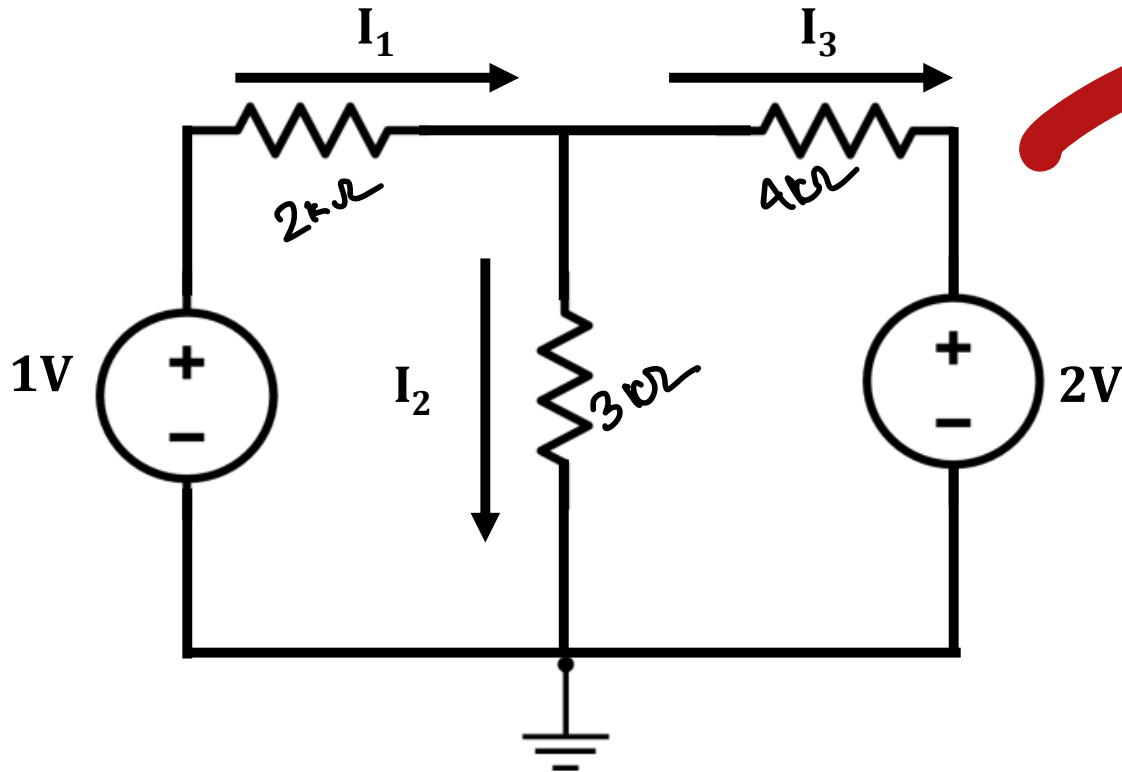- "The algebraic sum of all currents entering and exiting a node must equal zero."
- "Currents flowing into a node (or a junction) must be equal to the currents flowing out of it."




$$I_1 = I_2 + I_3$$


$$\frac{1 - v_1}{R_1} = \frac{v_1 - 2}{R_3} + \frac{v_1 - 0}{R_2}$$

*This is also applicable for supernodes!

Nodal analysis:

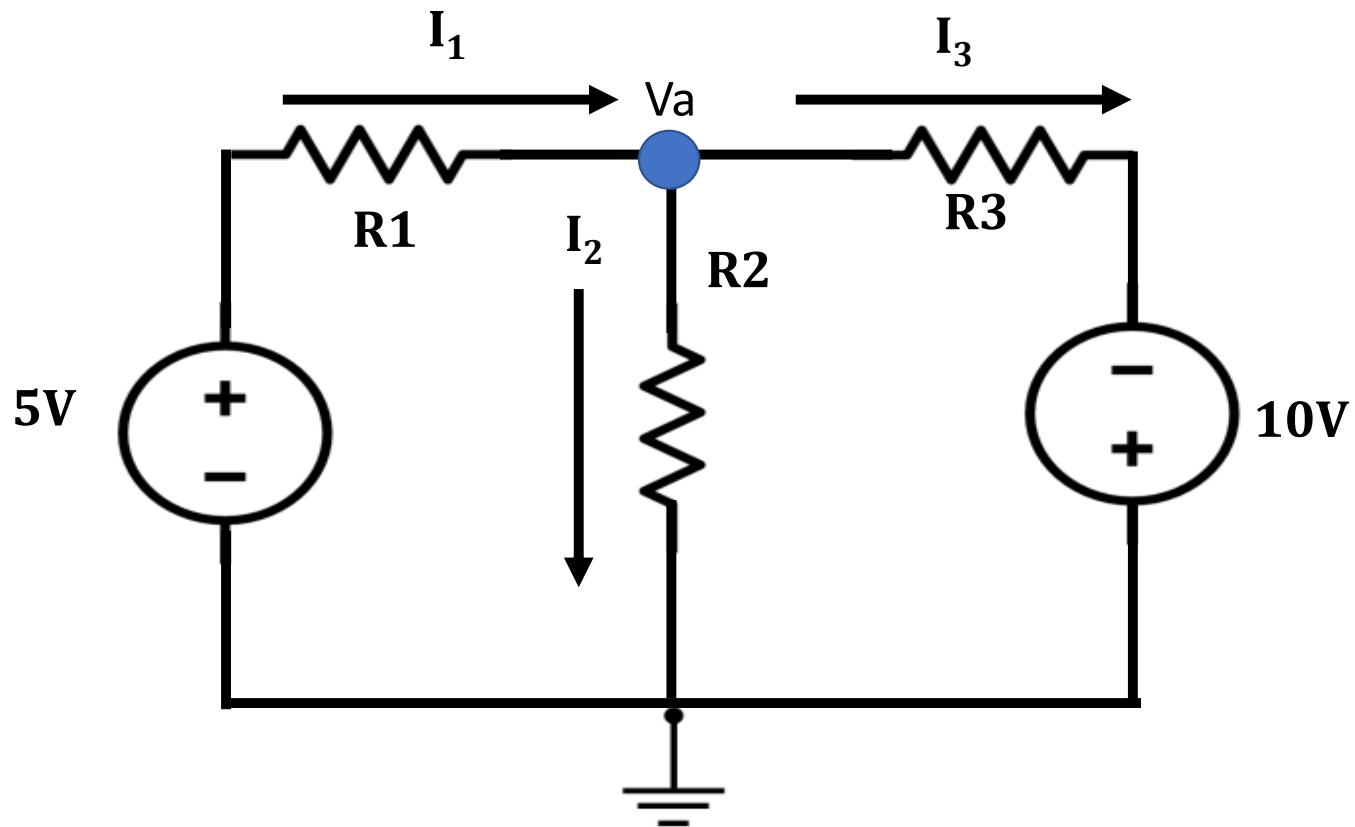


Do it by yourself:

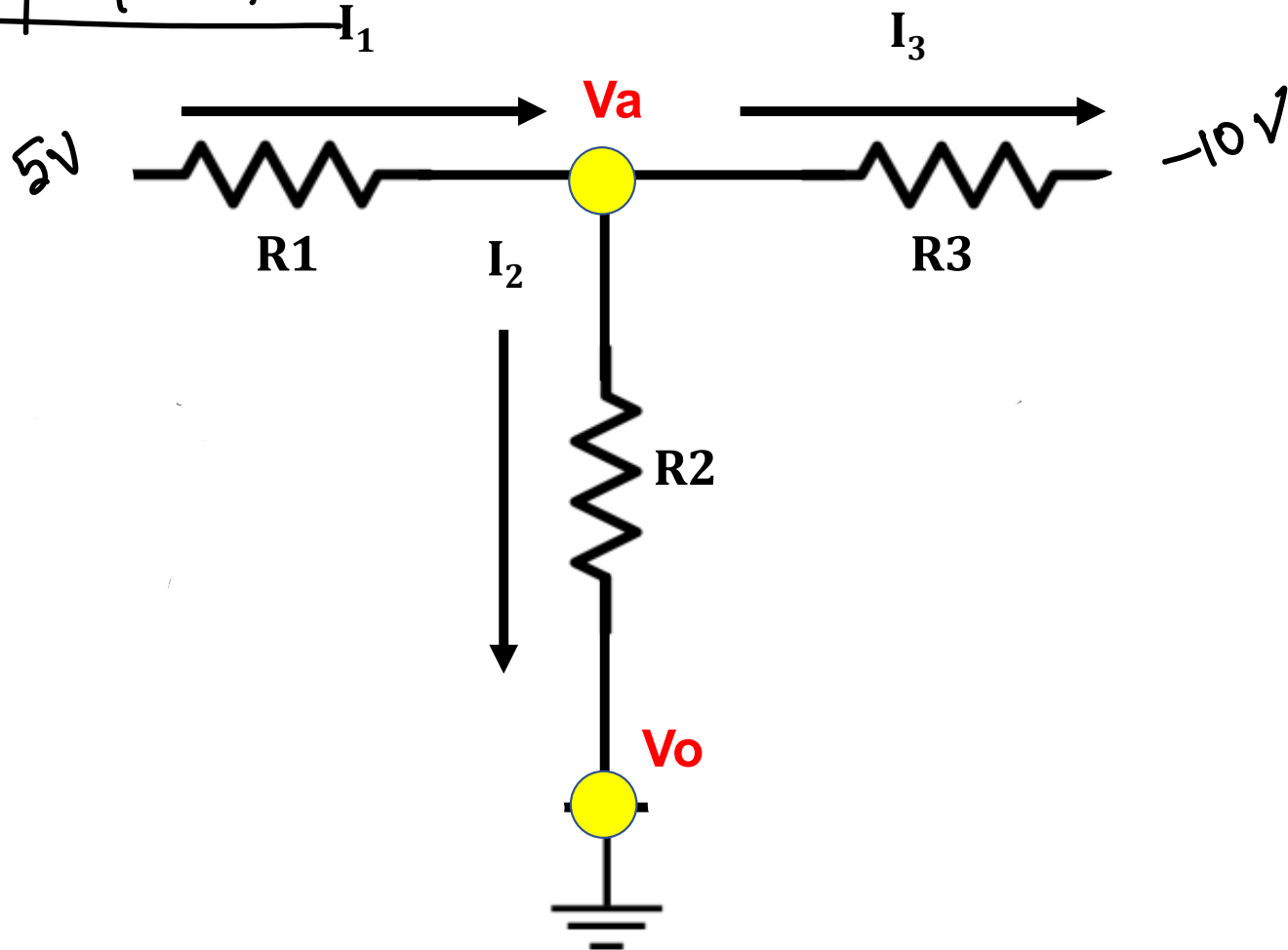


Kirchhoff's Voltage Law (KVL): The algebraic sum of all voltages in a loop must equal zero

$$-5 + I_1 R_1 + I_1 R_2 - I_2 R_2 = 0$$

$$I_2 (R_2 + R_3) - 10 - I_1 R_2 = 0$$

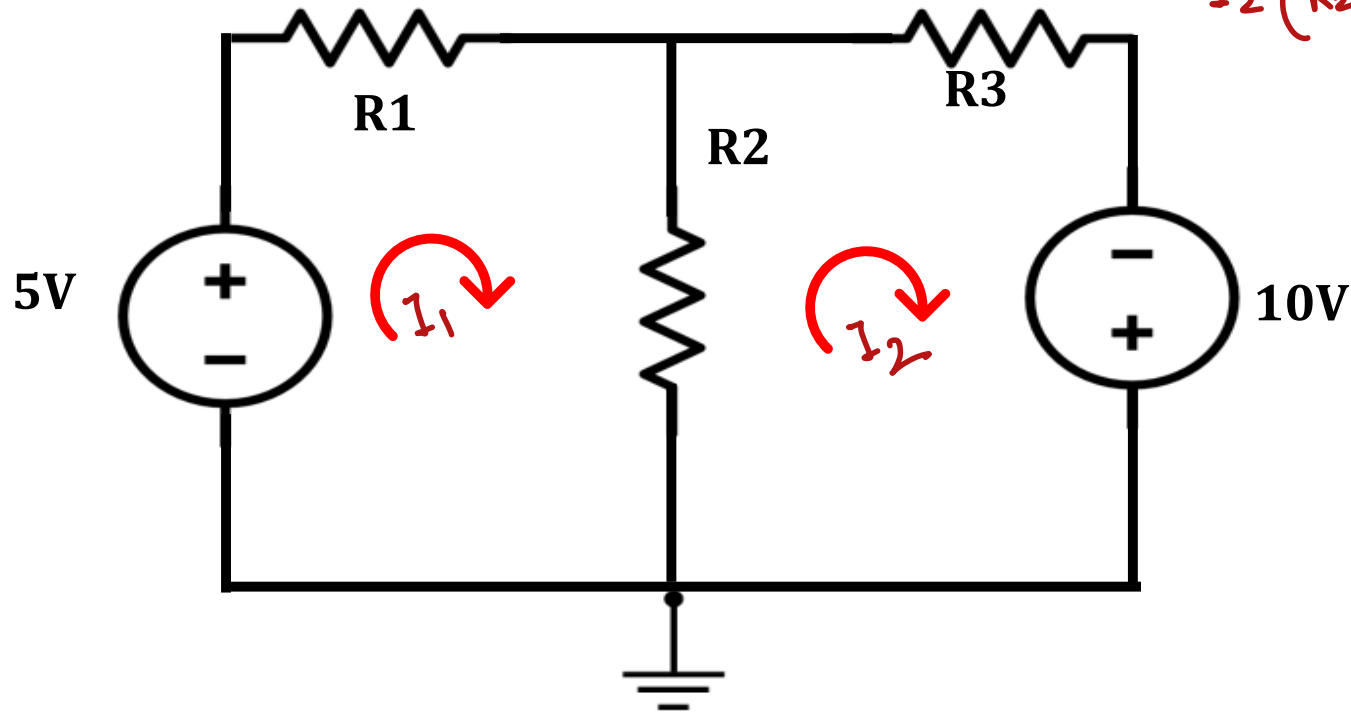
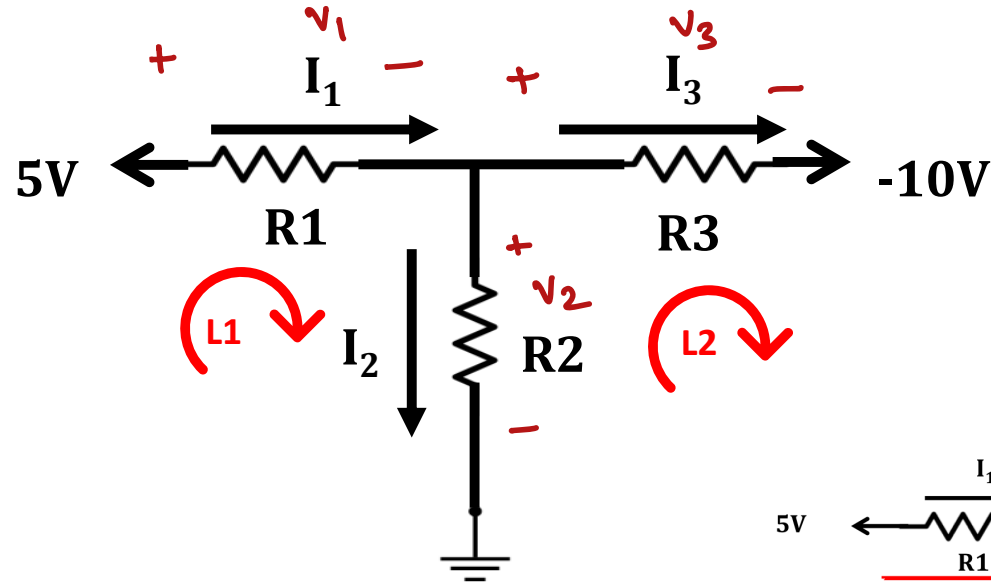
$$\sum V [\text{along line}] = \text{Voltage at the starting of the node} - \text{Voltage at the ending of the node}$$




$$V_1 = I_1 R_1$$


$$V_2 = I_2 R_2$$

$$V_3 = I_3 R_3$$

$$\text{Line 1: } 5 - 0 = I_1 R_1 + I_2 R_2 = 0$$
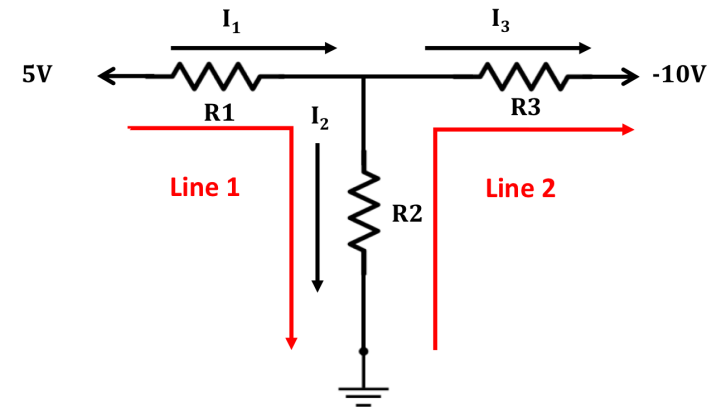
$$\text{Line 2: } 0 - 10 = -I_2 R_2 + I_3 R_3$$




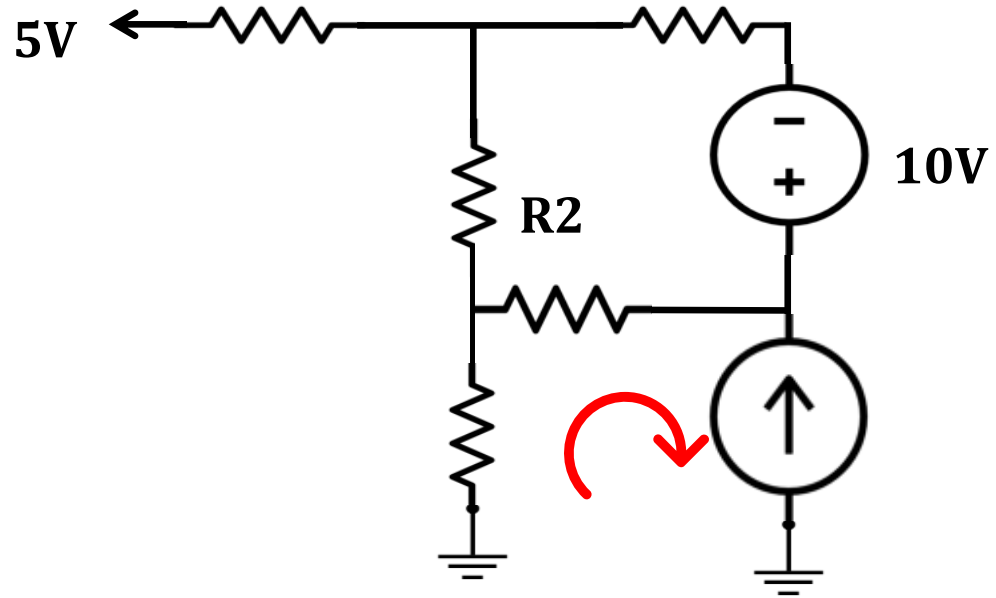





Can you write a KVL equation along this line?

Nodal analysis:
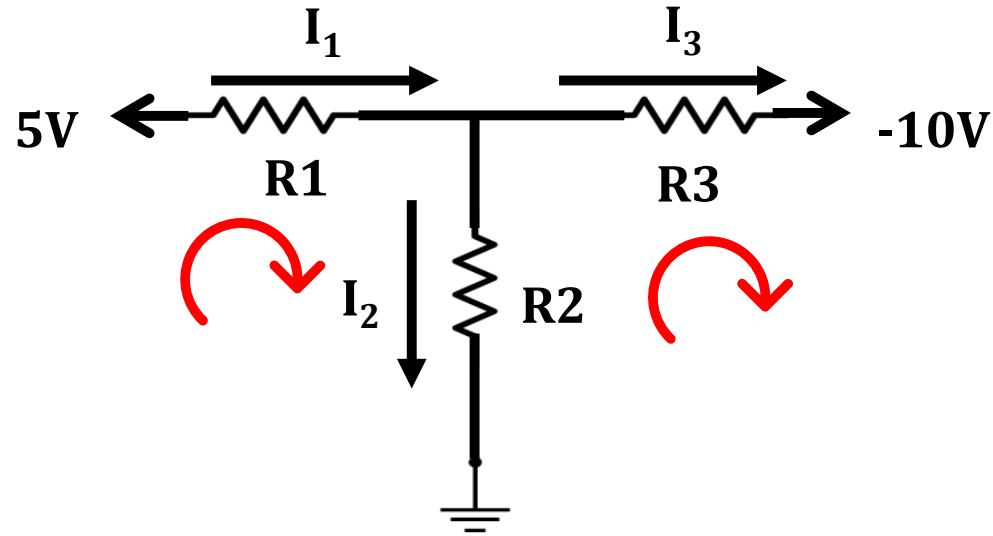
$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{5}{R_1} - \frac{0}{R_2} - \frac{-10}{R_3} = 0$$





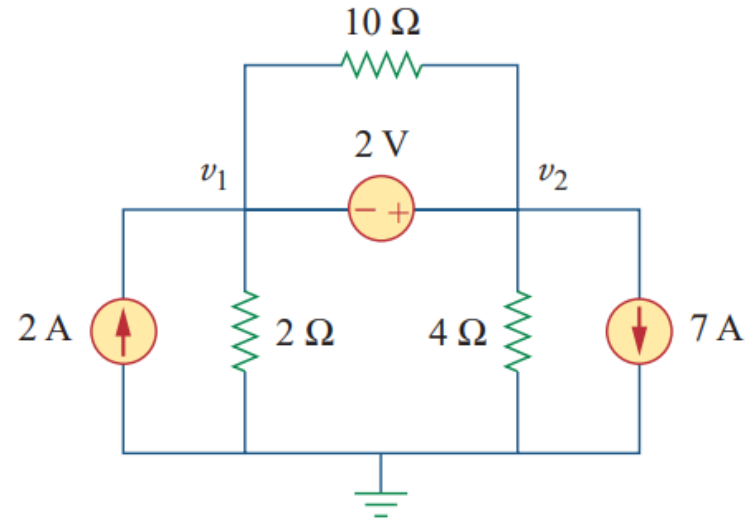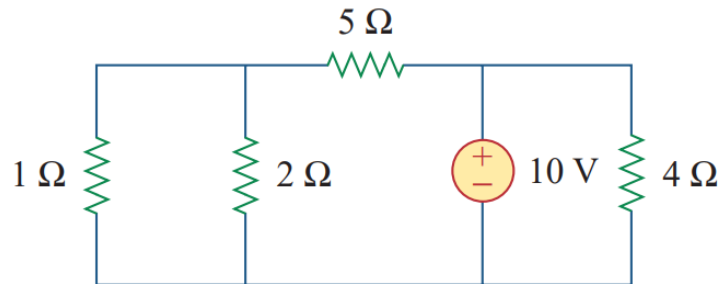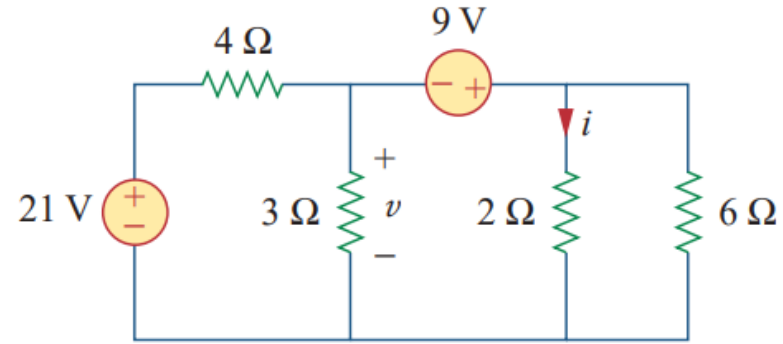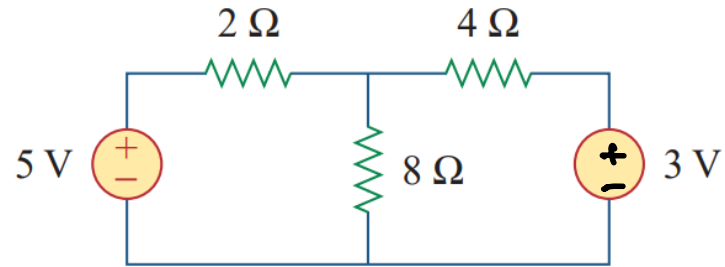Practice Problems: i) Draw Alternative Circuit Diagrams , ii) Write down KCL equations, iii) Write down KVL equations and iv) Nodal equation



Practice Problems

① Question:

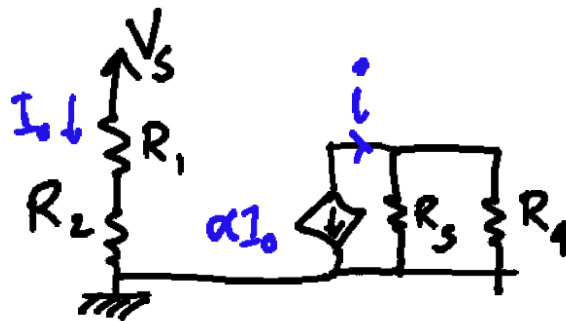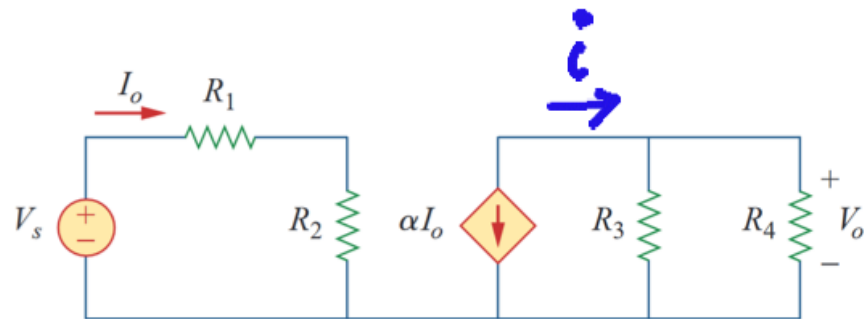

For the circuit, find $\left| \frac{V_o}{V_s} \right|$ in terms of α, R_1, R_2, R_3 and R_4 .

If $R_1 = R_2 = R_3 = R_4$ what value of α will produce $\left| \frac{V_o}{V_s} \right| = 10$?

Solution:


Ohm's Law across $R_1 + R_2$.

$$I_o = \frac{V_s}{R_1 + R_2}$$

$$i = -\alpha I_o$$

Voltage across **Parallel Resistors** R_3, R_4


$$V_o = i(R_3 || R_4) = -\frac{\alpha V_s}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

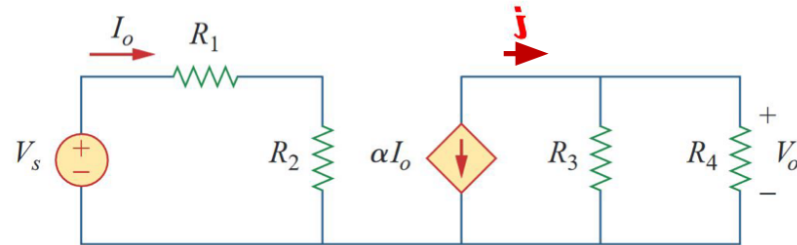

$$\left| \frac{V_o}{V_s} \right| = \frac{\alpha}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$


$$\alpha = 40$$


② Question :

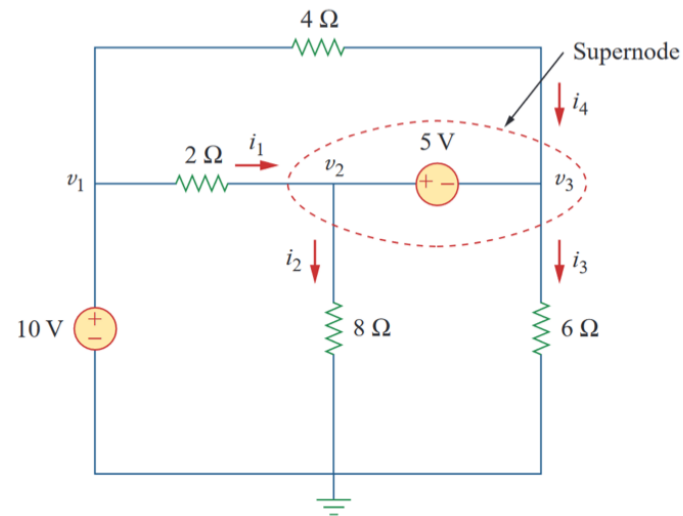

Write down the node equations.

Solution:

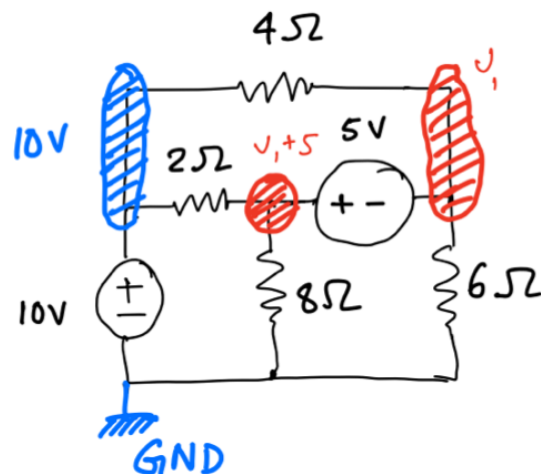

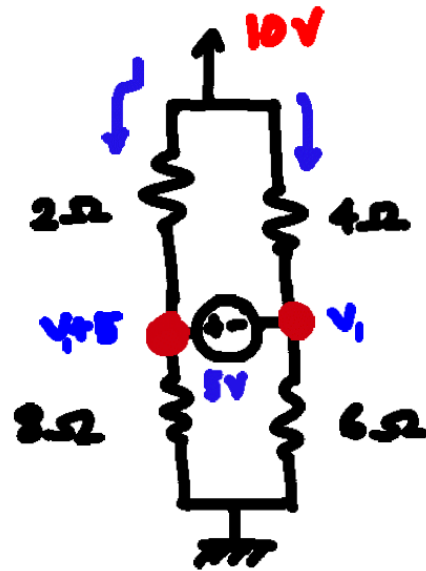

Node equation for node v_1


$$v_1 \left(\frac{1}{4} + \frac{1}{6} \right) + (v_1 + 5) \left(\frac{1}{2} + \frac{1}{8} \right) - 10 \left(\frac{1}{2} + \frac{1}{4} \right) = 0$$

③ Question: find I_1


KCL at node v_o

$$\frac{0.6 - 0.5}{5} = \frac{(0.5 - 0.7) - (-0.5)}{10} + I_1$$

$$I_1 = -0.01 \text{ mA}$$

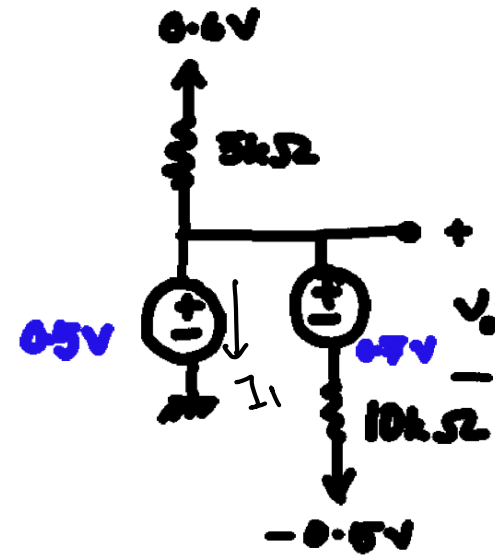

Q4) Question:

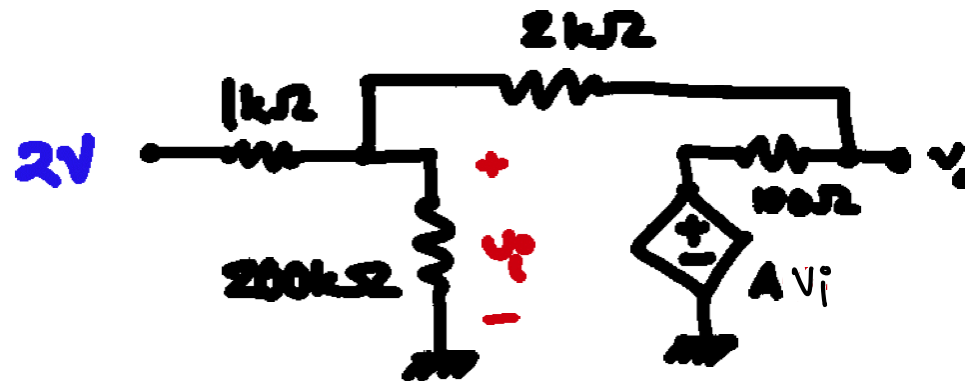

$$A = 2 \times 10^5$$

Solution:

KCL at node v_i

$$\frac{2 - v_i}{1} = \frac{v_i - v_o}{2} + \frac{v_i}{200}$$


$$\frac{301}{200} v_i - \frac{1}{2} v_o = 2$$

KCL at node v_o

$$\frac{v_i - v_o}{2} + \frac{A v_i - v_o}{0.1} = 0$$

$$(2 \times 10^6 + 0.5) v_i - 10.5 v_o = 0$$

5 Question:

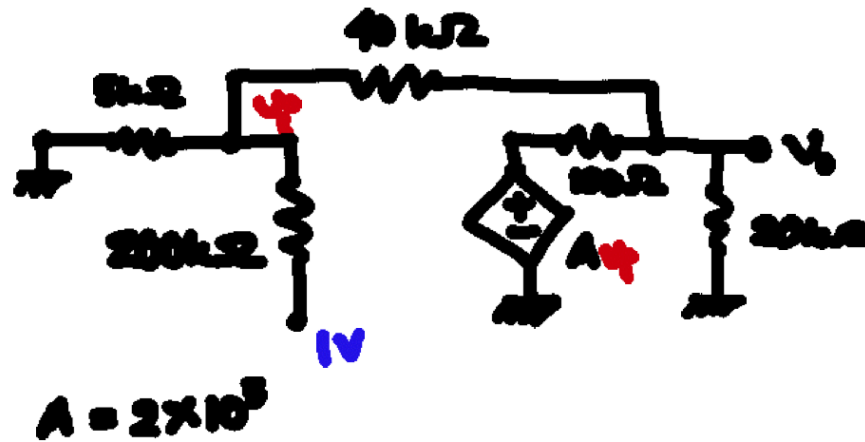

KCL at node v_i

$$\frac{0 - v_i}{5} = \frac{v_i - v_o}{40} + \frac{v_i - 1}{200}$$

$$\frac{23}{100}v_i - \frac{1}{40}v_o = \frac{1}{200}$$

KCL at node v_o

$$\frac{v_i - v_o}{40} + \frac{Av_i - v_o}{0.1} = \frac{v_o}{20}$$

$$(2 \times 10^6 + 0.025)v_i - 10.075v_o = 0$$

6 Question:


For $R = 100\ \Omega$, $R_L = 10\ \text{k}\Omega$, $r_z = 20\ \Omega$, $V_{ZO} = 3\ \text{V}$, and $I_Z = 1\ \text{mA}$.

a. Find V_O

b. Find I_L

c. Find I

d. Find V^+

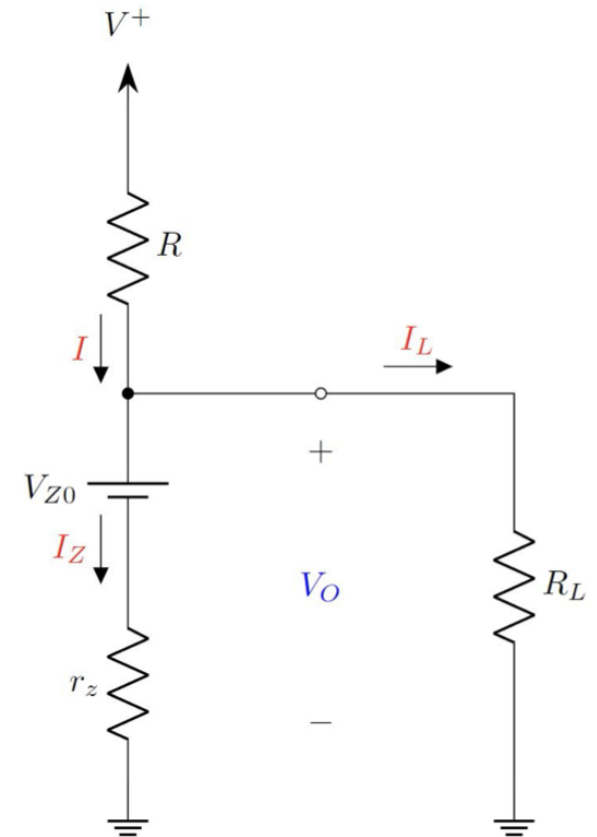


$$V_z = 20 \times 1\text{m} = 20\text{mV}$$

$$V_o = 3\text{V} + V_z = 3.002\text{V}$$

$$I_L = \frac{V_o}{R_L} \text{ mA}$$


$$I = I_z + I_L$$

$$\frac{V_+ - V_o}{100} = I$$

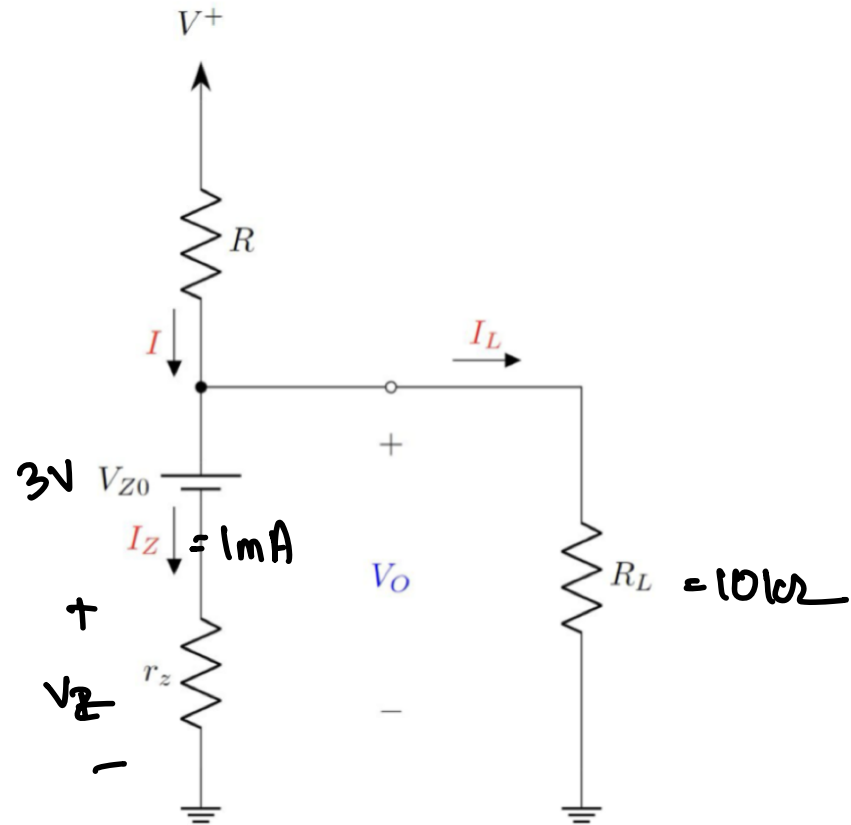


⑦ Question:

find i_a

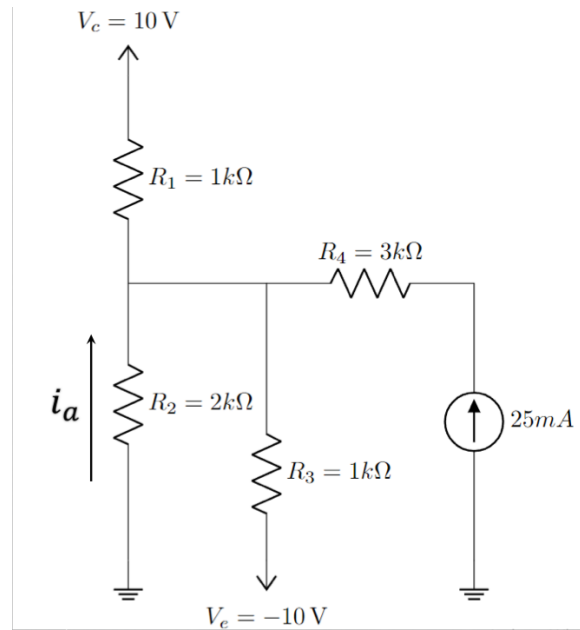

Solution:

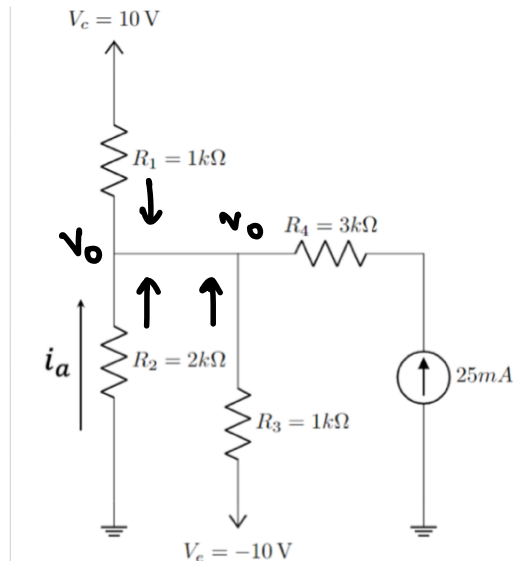

$$\frac{10 - V_o}{1k} + \frac{0 - V_o}{2k} + \frac{-10 - V_o}{1k} + 25mA = 0$$

$$i_a = \frac{0 - V_o}{2k}$$