


Set - A Quiz - 2

b

D_1, D_2 cannot be ON at same time as otherwise

V_{ab} would receive $0.7V$ and $-0.7V$ drop at same time \rightarrow impossible case!

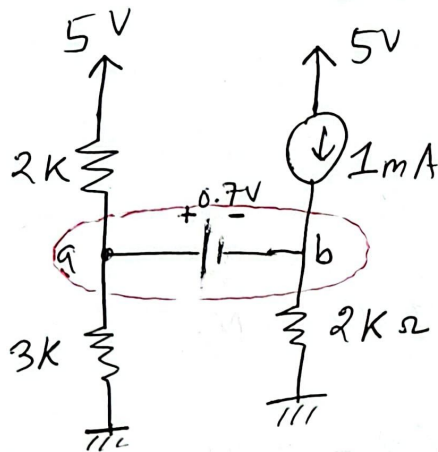if $D_1 = \text{ON}, D_2 \rightarrow \text{off} :$



at super node:

$$\frac{V_a - 5}{2} + \frac{V_a}{3} + \frac{V_b}{2} - 1 = 0$$

$$\Rightarrow 3V_a - 15 + 2V_a + 3V_b - 6 = 0 \quad \text{--- (1)}$$

$$\text{and, } -V_a + 0.7 + V_b = 0 \quad \text{--- (2)}$$

$$\text{solving} \rightarrow V_a = 2.8875V$$

$$V_b = 2.1875V$$

$$\text{Hence, } I_{ab} = \text{apply KCL at node } a = \frac{5 - V_a}{2K} + \frac{0 - V_a}{3K} \\ = 0.09375 \text{ mA}$$

As we assumed D_1 to be on and $0.09375 \text{ mA} > 0$

hence, our assumption is true and correct for D_1 .

$$\text{As for } D_2 \rightarrow V_{ba} = V_b - V_a = -0.7V \neq 0.7V$$

hence D_2 is off as assumed.

① if both diodes disconnected:

$$V_a = 5 \times \frac{3}{3+2} = 3V$$

$$V_b = 2K \times 1m = 2V$$

9 UP
⑥ If two diodes are in opposite direction in series then overall network is off

$$\text{Hence } \boxed{I_{ab} = 0 \text{ A}}$$

Question No. 2

⑨ for D1 and D2 \rightarrow both can't be ON.

if D1 ON, D2 off: $V_{01} = (2 - 0.3) = 1.7 \text{ V}$
 \downarrow

$V_{01} = 1.7$ doesn't turn on D2 as
 $(2.2 - 1.7) = 0.5 \text{ V} < V_{D2}$

Hence assumption ok $\rightarrow V_{01} = 1.7 \text{ V}$

for D3, D4: both can't be ON.

if D3 ON, D4 off $\rightarrow V_{02} = (2.4 - 0.5) = 1.9 \text{ V}$

as for D4 $\rightarrow (2.5 - 1.9) = 0.6 \text{ V} < V_{D4}$

hence, assumption ok \rightarrow D4 stays off. $V_{02} = 1.9 \text{ V}$

(b) $V_{DD} = 5V$ here. $V_{o1} = 1.7V$, $V_{o2} = 1.9V$

analyze before any current flow occurs in $D_5, D_6 \rightarrow$

D_5, D_6 can't stay ON at same time ^{as} V_o would receive 2 different node voltages.

if D_5 ON, D_6 off :

$$V_o = V_{D5} + V_{o1} = 1 + 1.7 = 2.7V$$

$$\text{for } D_6 \rightarrow (V_o - V_{o2}) = (2.7 - 1.9) = 0.8V < 1V$$

hence, D_6 stays off as assumed.


$$\text{Hence, } \boxed{V_o = 2.7V}$$

(c) if $V_3 = -2V$, $V_4 = -3V$:

~~D_3 ON, D_4 off $V_{o2} = -2V$ $V_{o1} = -3.5V$~~

No diode can get ON because D_3, D_4 both are in reverse biased state.

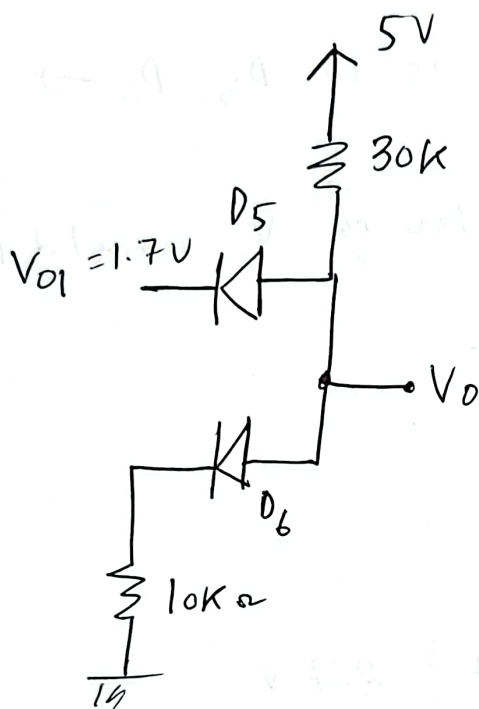from ① $\rightarrow V_{01} = 1.7V$, ~~0.005045 A~~



if D_5 ON, D_6 off $\rightarrow V_0 = 1.7 + 1 = 2.7V$

↓
turns on D_6 as well.

Hence, D_5 can't be ON.

if $D_5 = \text{off}$, $D_6 = \text{ON}$:

$$I_{D6} = \frac{5 - V_{D6}}{10K + 30K} = 0.1 \text{ mA}$$

$$\text{hence, } V_0 = KVL = (0.1 \text{ mA} \times 10K) + V_{D6} = 2V$$

$V_0 = 2V \rightarrow$ does not turn D_5 ON as $(2 - 1.7) < V_{D5}$

Hence this assumption \rightarrow correct.

$$V_o = 2V.$$