

ID:	Name:
-----	-------



**Brac University**  
Semester: Fall 2024  
Course Code: CSE251  
Electronic circuitry and devices  
Section:09  
Faculty: RMT


Set  
**A**

Assessment: *Quiz 1*  
Duration: 30 minutes  
Date: November 26, 2024  
Full Marks: 20

- ✓ **All questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.
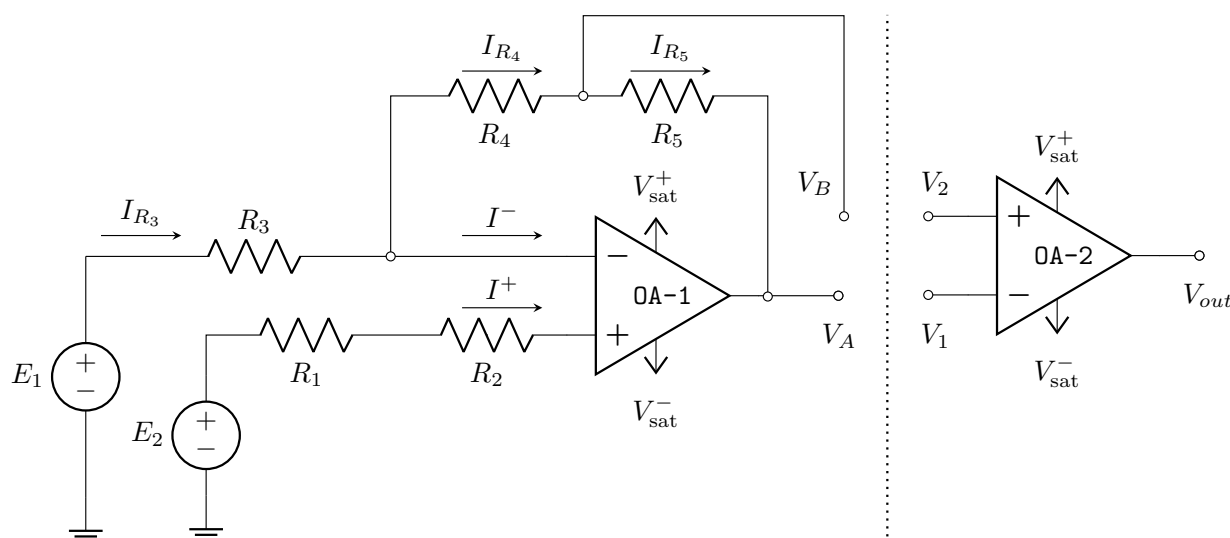
### ■ Question 1 of 2 [CO1, CO2, CO3] [10 marks]


The 'ideal' operational amplifiers (Op-Amp) below have been connected to saturation voltages  $V_{\text{sat}}^+ = +8\text{ V}$  and  $V_{\text{sat}}^- = -8\text{ V}$ . The resistor values are given as:  $R_1 = R_2 = 1\text{ k}\Omega$ , and  $4R_4 = 10R_5 = 20\text{ k}\Omega$ .



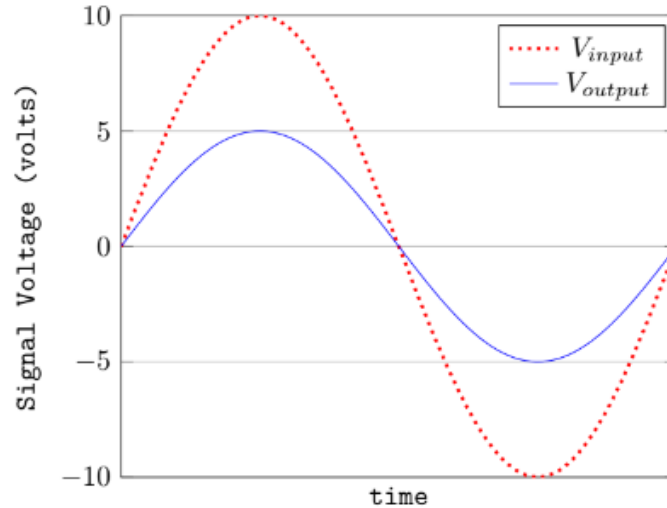- (a) [1 mark] **State** the current values of  $I^-$  and  $I^+$ .
- (b) [6 marks] If  $E_1 = 5\text{ V}$ ,  $E_2 = 0\text{ V}$ , and  $R_3 = 10\text{ k}\Omega$ , **determine**  $V_A$  and  $V_B$ .
- (c) [3 marks] **Find** the value of  $V_{\text{out}}$  if  $V_1 = V_A$  and  $V_2 = V_B$ .



Michael Scott wants to make a phone call to his assistant, Dwight Schrute, but the outdated phone system keeps failing as the signal is too weak by the time it reaches Dwight. Dwight plans on designing a device to help Michael make the call. The device will take the weak signal as input and give a strong signal at its output without changing the waveshape and polarity of the signal as shown in the following figure.



### ■ Question 2 of 2 [CO1, CO2, CO3] [10 marks]

- (a) [4 marks] Design circuit for the device based on the waveshapes in the figure shown above.
- (b) [6 marks] Dwight calculates his yearly sales using the following function. Design a device to help Dwight implement the function,  $f$

$$f = -3 \frac{dx}{dt} + 6x + 9 \int y \, dt \quad (1)$$

where  $x$ ,  $y$ , and  $z$  will be the inputs of the device.

