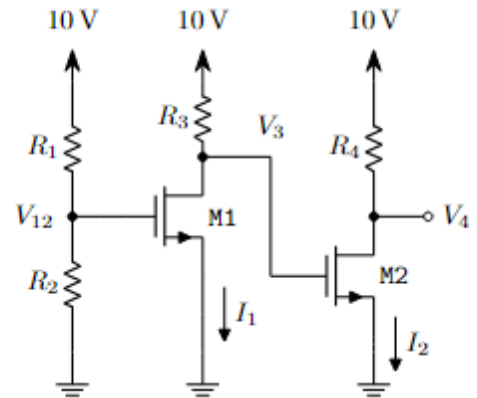


Relevant information for the circuit configuration on the right is given in the tables below:

Resistor values in ( $k\Omega$ )			
$R_1$	$R_2$	$R_3$	$R_4$
3	5	2	4

Transistor Parameters
$k_n = 2 \text{ mA/V}^2$
$V_T = 1 \text{ V}$



- [CO1] Draw the IV-characteristics of a MOSFET using S-model with proper labeling. [1]
- [CO2] Determine the value of  $V_{12}$ . [1]
- [CO2] Calculate the value of drain-to-source voltage of the transistor M1. In the process, determine the operating mode of M1. [3.5]
- [CO2] Determine which one of the four resistors will consume the least amount of power. [Hint, Power =  $I^2 R$ ] [3]
- [CO2] Determine how the operating mode of M2 would change if  $R_2$  were set to zero. [1.5]

**Solution:**

$$V_{12} = \frac{R_2 \times 10}{R_2 + R_1} = 6.25 \text{ V}$$

**Solution:** For **triode** mode of operation:

$$\begin{aligned}
 V_{OV} &= V_{GS} - V_T = 5.25 \text{ V} \\
 I_1 &= \frac{10 - V_3}{R_3} = k(V_{OV}V_3 - \frac{V_3^2}{2}) \\
 \frac{10 - V_3}{2} &= 2(5.25V_3 - \frac{V_3^2}{2}) \\
 \frac{1}{2}V_3^2 - 5.5V_3 + 2.5 &= 0 \\
 V_3 &= 0.48 \text{ V} < V_{OV}
 \end{aligned}$$

So, the MOSFET is operating in **triode** mode.

**Solution:** As  $V_3 = 0.48 \text{ V} < V_T$ , the MOSFET M2 is in **cut-off**. So,  $I_2 = 0$ . So, no power is consumed by  $R_4$ . Therefore,  $R_4$  consumes the least power.

**Solution:** When  $R_2 = 0 \Omega$ , the MOSFET M1 is in **cut-off** as the gate terminal is shorted to ground. So,  $V_3 = 10 \text{ V}$ . So, the MOSFET M2 would change its mode from **cut-off** to **triode**.