

# Assignment-1

## Op-Amp

1.

A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure in a water tank. The valve operates on **ACTIVE LOW** logic. (i.e., the valve is OPENED when given a LOW voltage of 1 V, but remains CLOSED when provided a HIGH voltage of 6 V.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.


At <b>0.5 atm</b> pressure	At <b>1 atm</b> pressure	At <b>1.5 atm</b> pressure
$v_{0.5 \text{ atm}} = 0.5 \text{ V}$	$v_{1 \text{ atm}} = 3 \text{ V}$	$v_{1.5 \text{ atm}} = 5.5 \text{ V}$

The pressure in the water tank can be measured by the formula  $P = h\rho g$ , where  $P$ , (in **Pascals (Pa)** unit) is the water pressure,  $h$  is the height of water in the tank (in *metres*),  $\rho (= 1000 \text{ kgm}^{-3})$  is the density of water and  $g$  is the acceleration due to gravity (in  $\text{ms}^{-2}$ ).


[1 atm = 101325 Pa]

- Design** a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds **10 m**.
- Draw** the voltage transfer characteristics (VTC) of the designed Op-Amp.

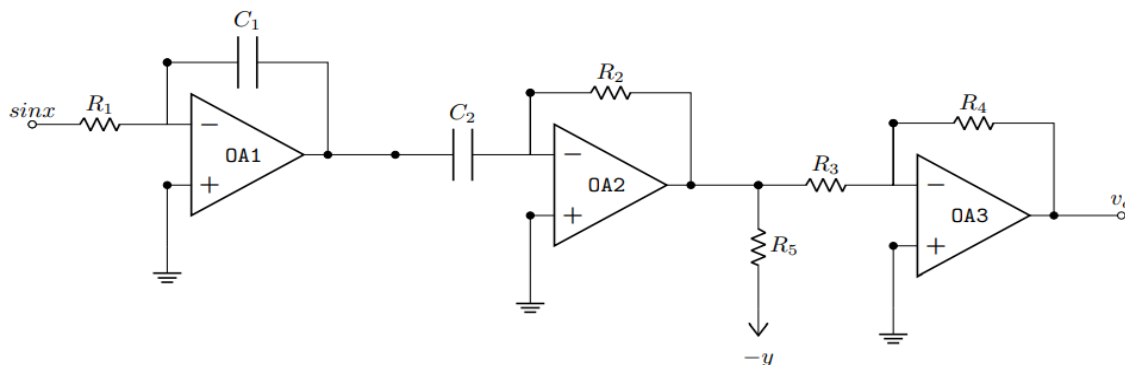2. **Deduce** the expression for output,  $V_o$  from the circuit above




3.

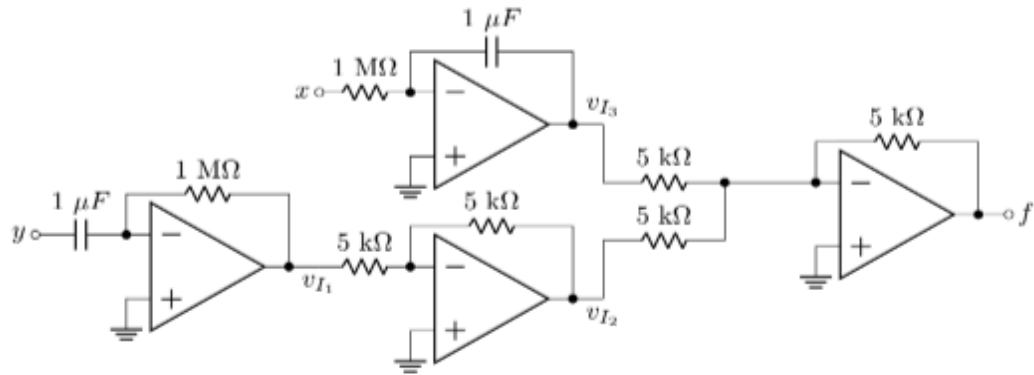


- Analyze** the circuit above to find an expression of  $f$  in terms of inputs  $x$  and  $y$ . Also, **determine** the intermediate outputs  $v_{I1}$ ,  $v_{I2}$ , and  $v_{I3}$  as denoted in the circuit. [4]
- Draw the circuit of an inverting amplifier and **design** it in such a way that the voltage gain,  $k = -4$ . (*i.e.*, find the values of  $R_1$  and  $R_2$ ). [3]
- Show** the input and output waveforms of the inverting amplifier of part (b) assuming a sinusoidal input of 0.5 V amplitude. **Calculate** the amplitude of the output. [2]
- Consider the inverting amplifier of part (b) again. Assume the input voltage can provide a maximum current of 0.5  $\mu\text{A}$ . **Determine** the design changes required, if any, for the circuit to work. [1]

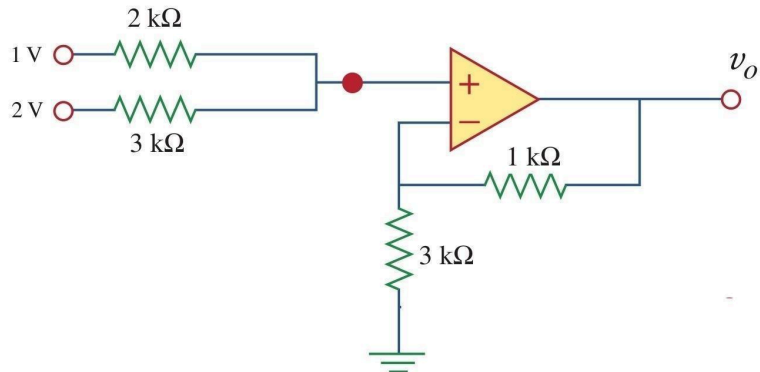
4. Consider the Ideal Op-Amp and find the value of  $V_o$ .



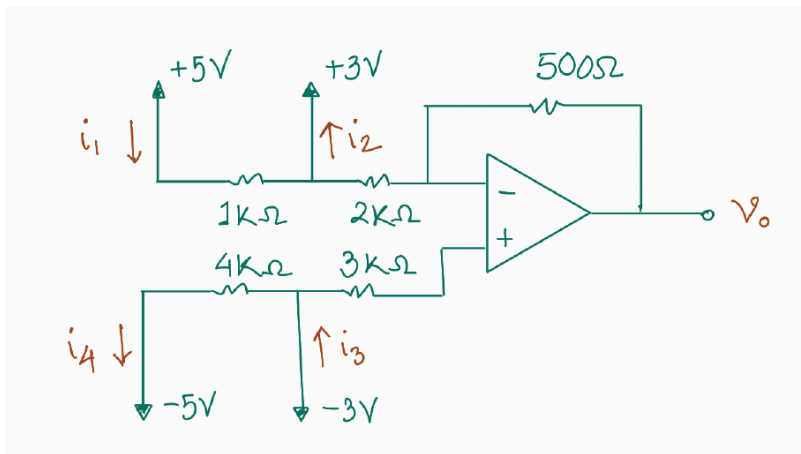
5. Determine the marked currents and the output voltage



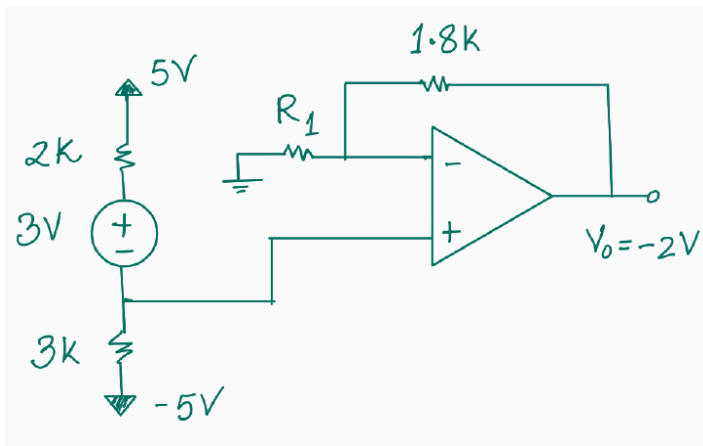
6. Determine the appropriate value of  $R_1$



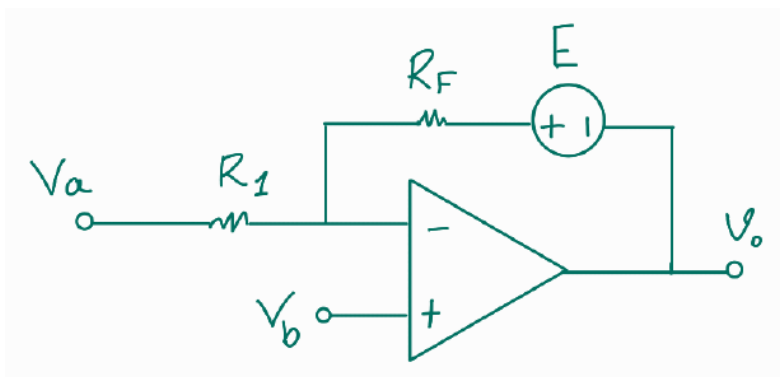
7. Express the output voltage  $v_o$  in terms of all the other quantities shown in the circuit below.



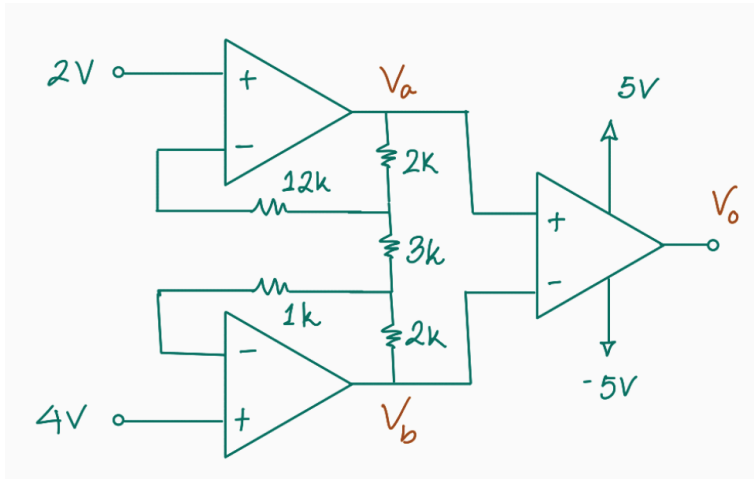8. Determine the output of the comparator,  $V_o$  after finding  $V_a$  and  $V_b$ .



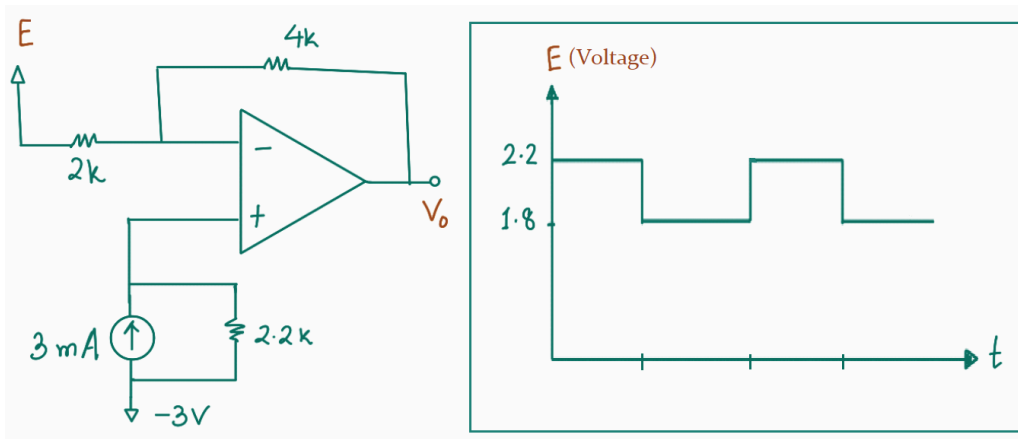9. Draw the correct waveform of  $V_o$  (with voltage labels) alongside the input waveform of  $E$ .



10. Draw the approximate waveforms of both  $V_A$  and  $v_o$  from the circuit below.

